

---

---

# **ANALYSIS OF POWER ELECTRONIC CONVERTERS DC/AC**

---

---



IOAKEIMIDOU PANAGIOTA

PAPADOPOULOS ANASTASIOS

TOUNA PANAGIOTA
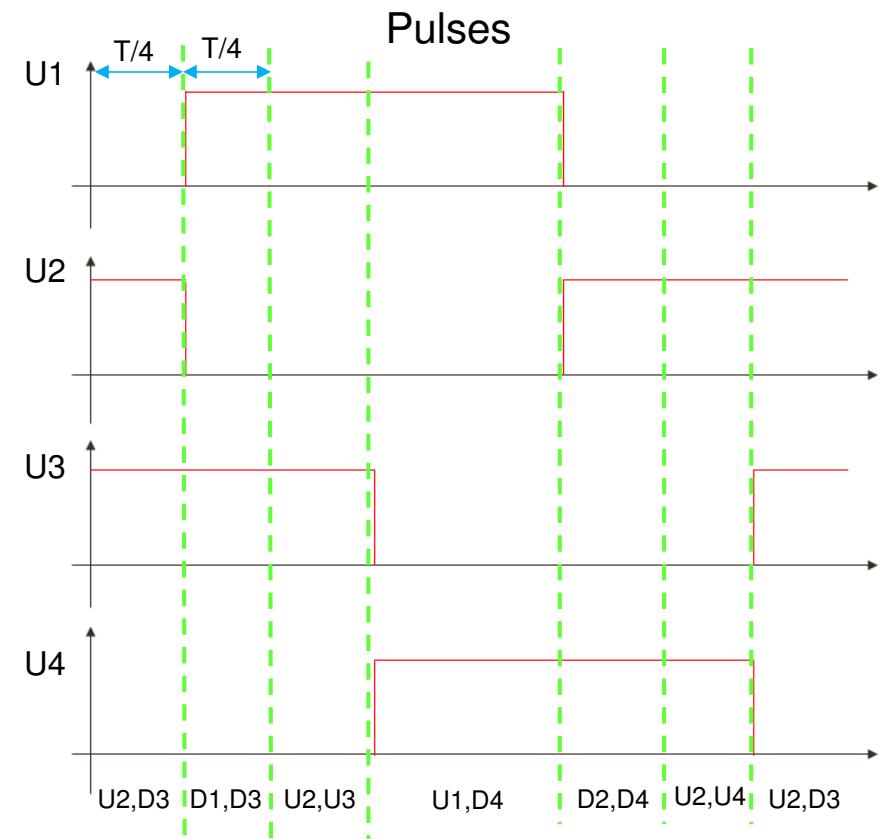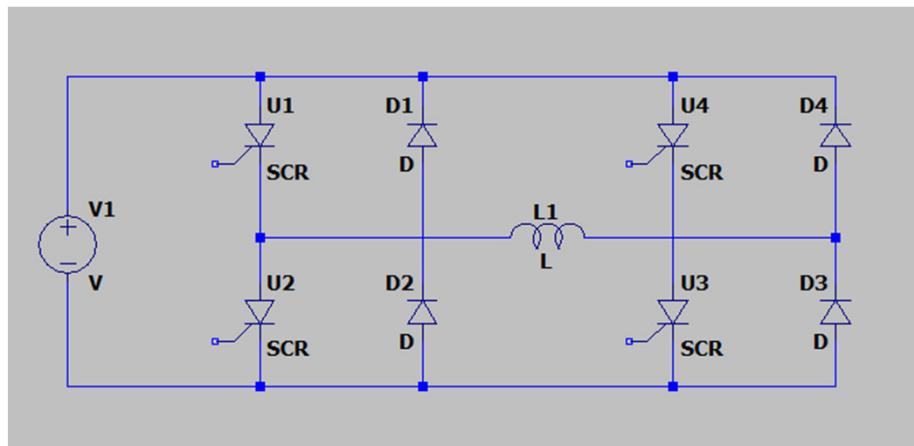
## Exercise 34

Analyse the operation of a square wave inverter with pure inductive load and pulse width of the output voltage equal to  $90^\circ$ .





### Operating States

State	$U_1$	$U_2$	$U_3$	$U_4$	$V_o$	$i_o$	$i_s$
1	0	1	1	0	0	ct	0
2	1	0	1	0	$V_d$	$\frac{di}{dt} > 0$	$i_o$
3	1	0	0	1	0	ct	0
4	0	1	0	1	$-V_d$	$\frac{di}{dt} < 0$	$i_o$



### Current Flow

State	$i_o > 0$	$i_o < 0$	Power Flow $i_o > 0$	Power Flow $i_o < 0$
1	$U_3, D_2$	$U_2, D_3$	Loop	Loop
2	$U_1, U_3$	$D_1, D_3$	Source $\Rightarrow$ Load	Source $\Leftarrow$ Load
3	$U_1, D_4$	$U_4, D_1$	Loop	Loop
4	$D_2, D_4$	$U_2, U_4$	Source $\Leftarrow$ Load	Source $\Rightarrow$ Load



**U2,D3**

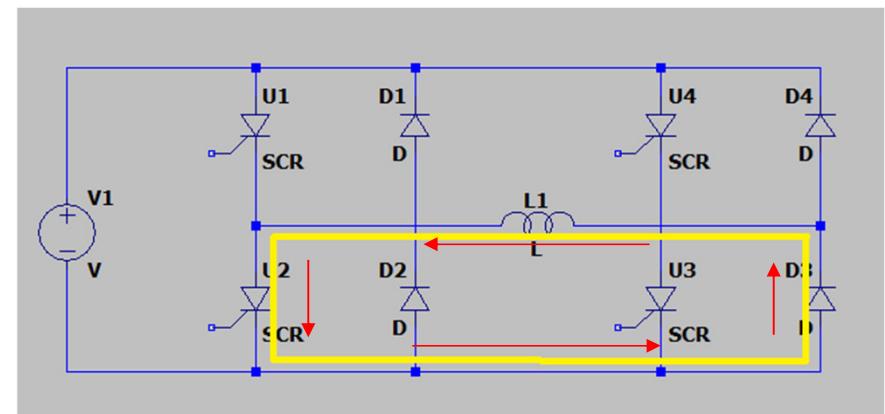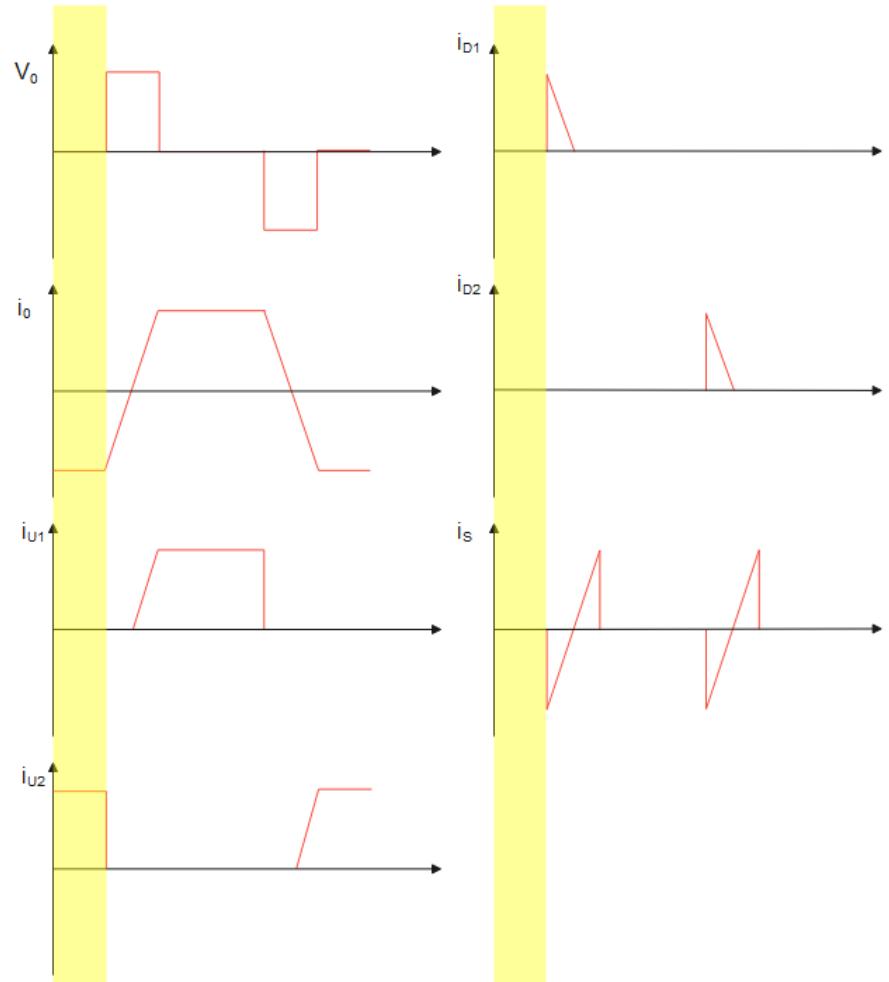



# D1,D3

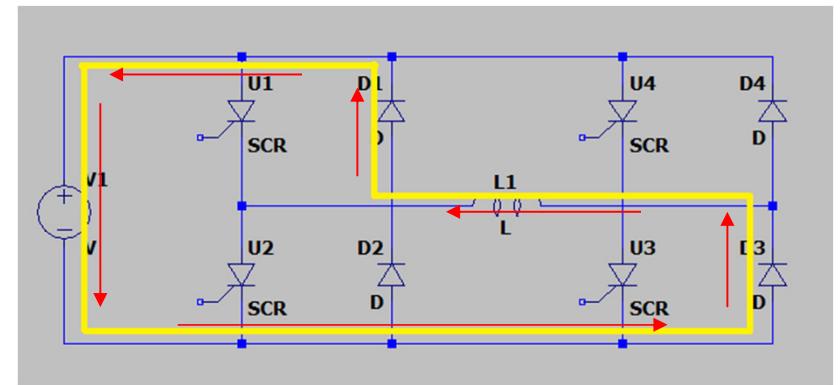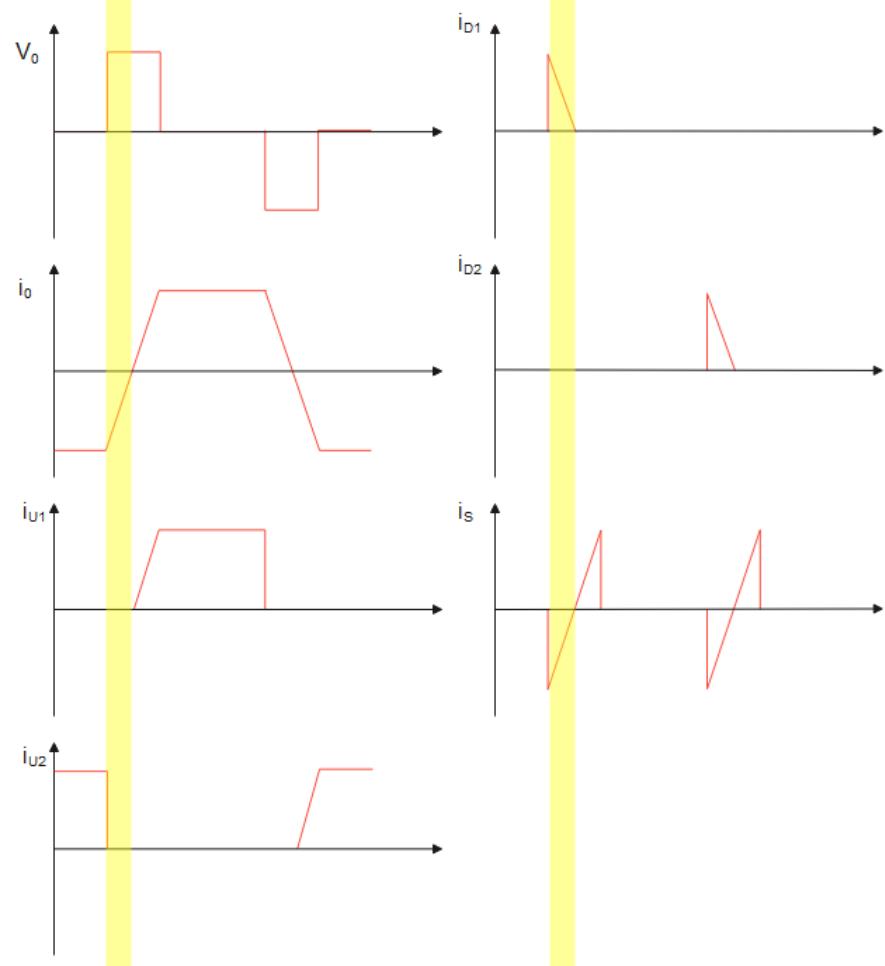



# U1,U3

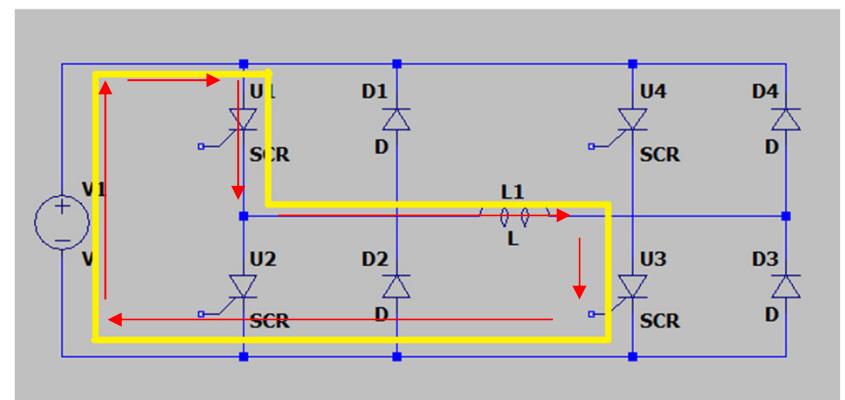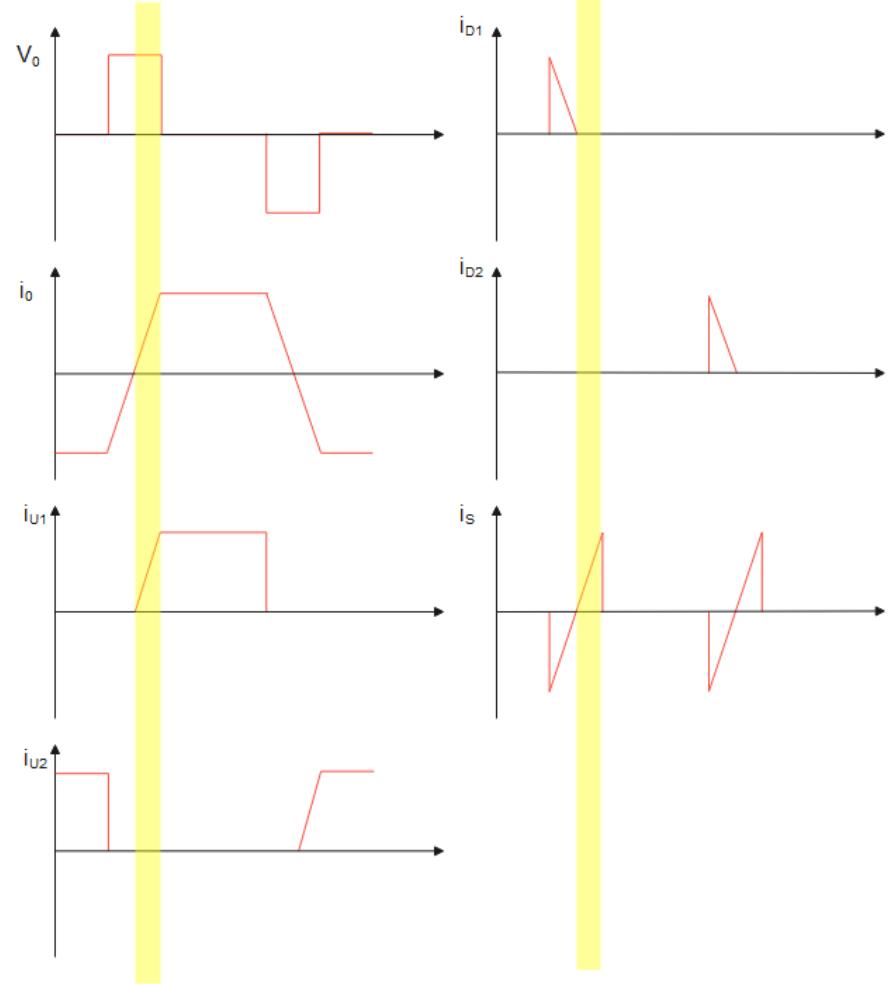



**U1,D4**

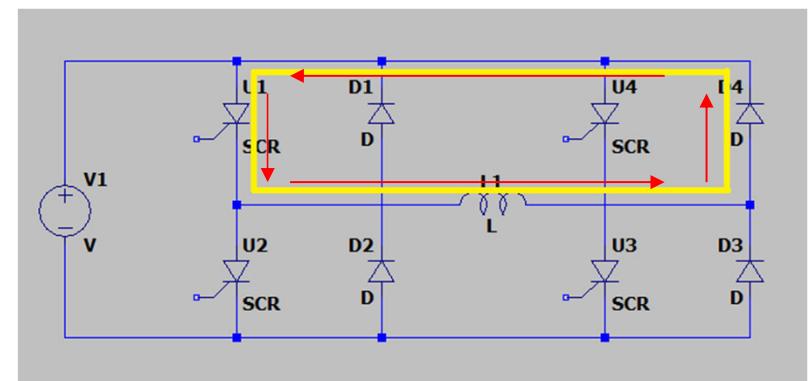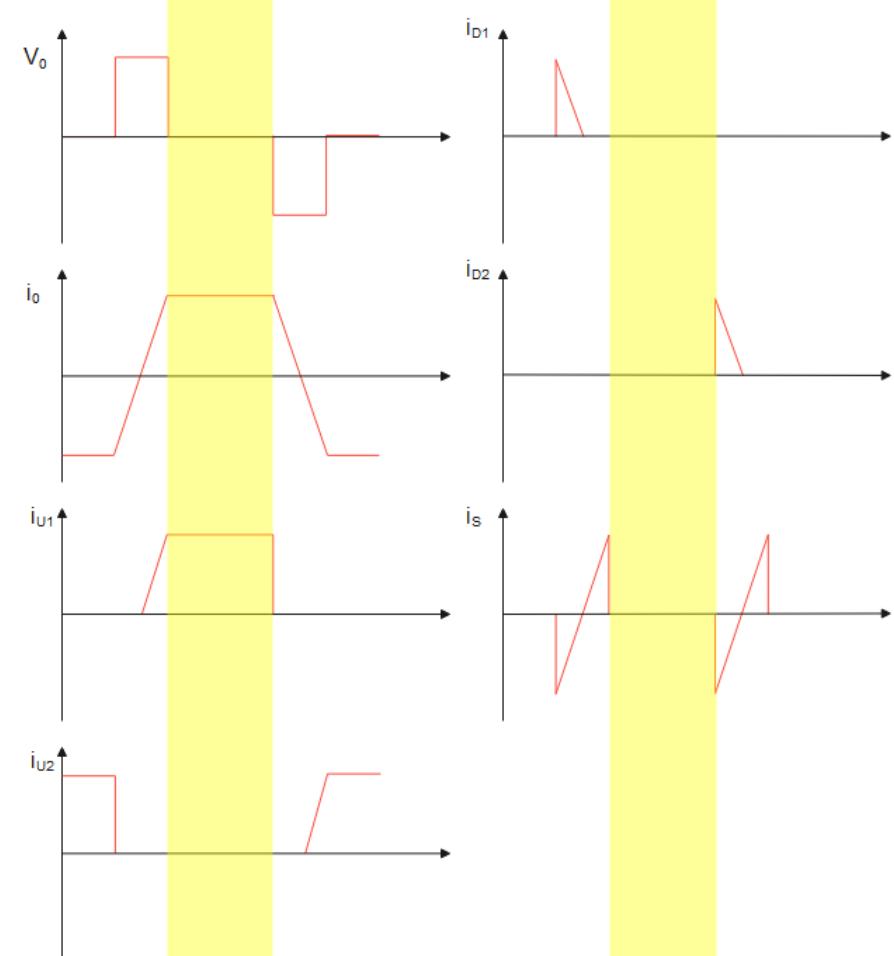

D2,D4

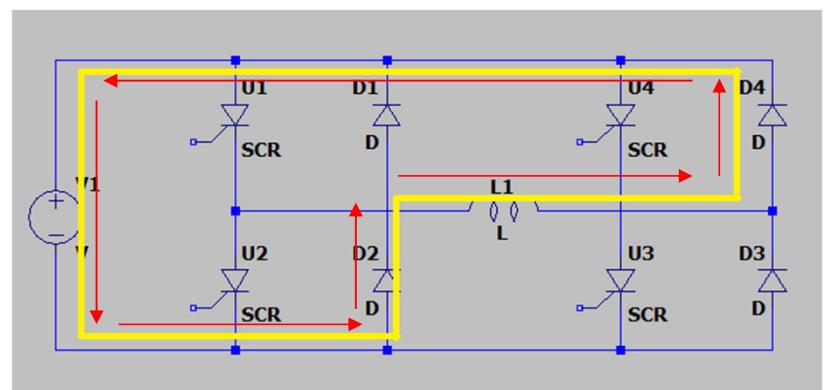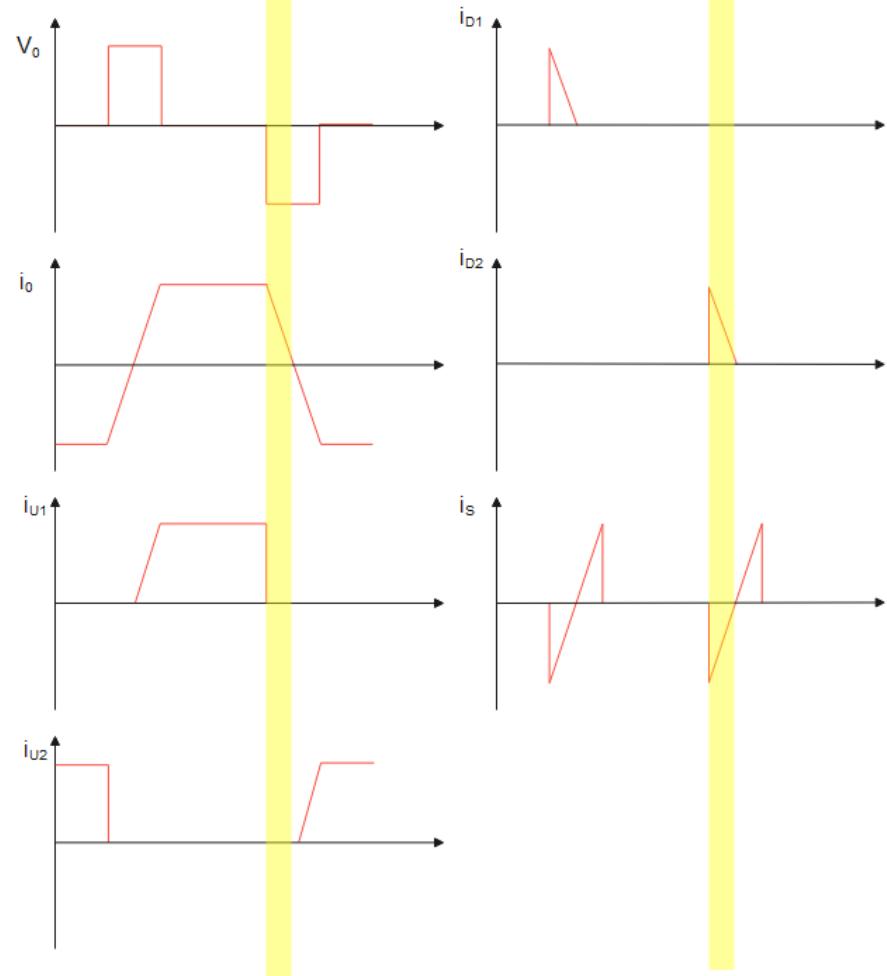

# U2,U4

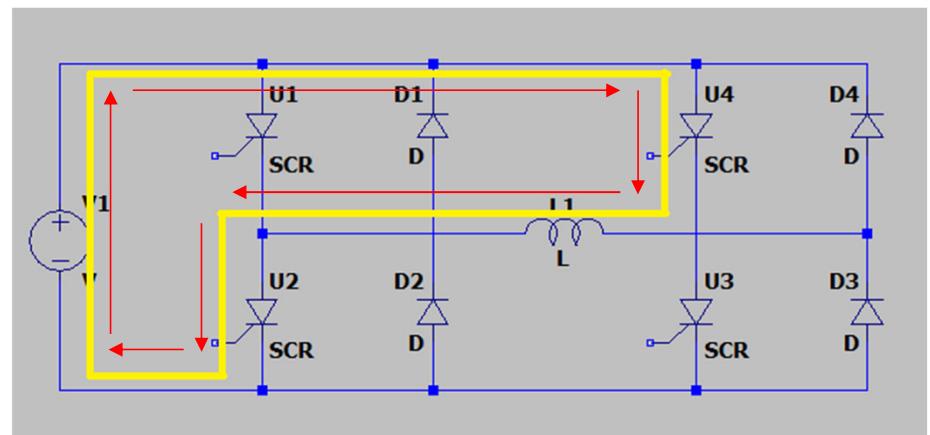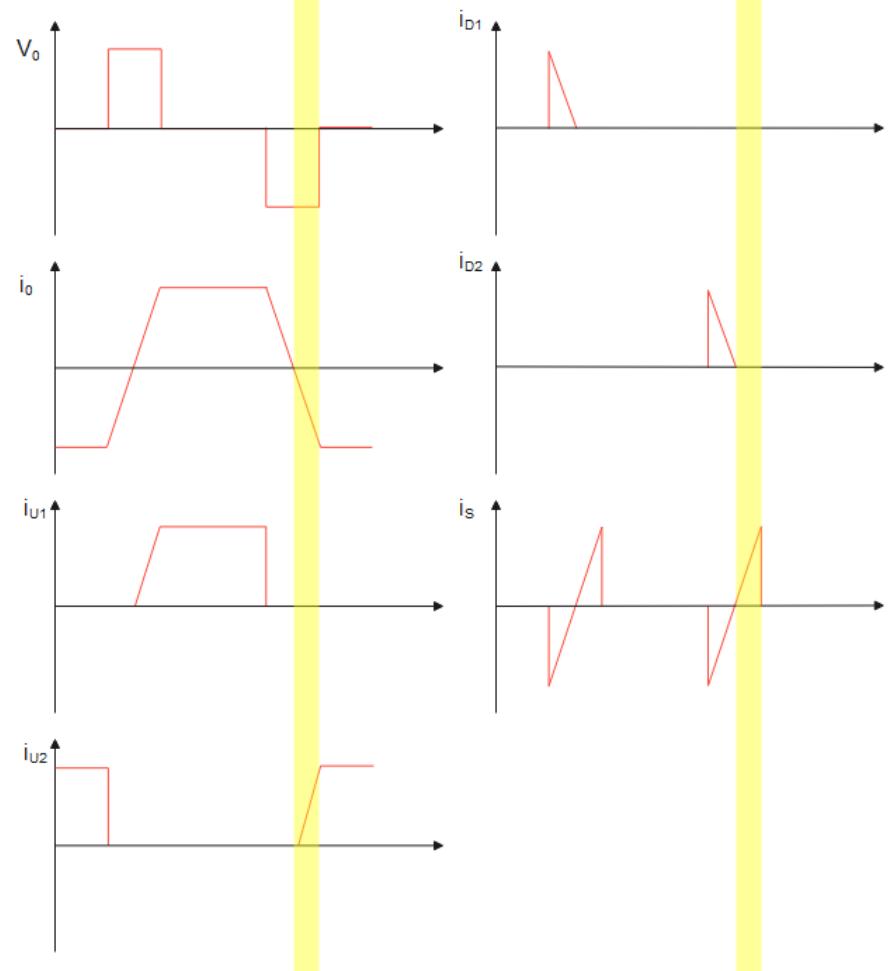

# U2,D3

