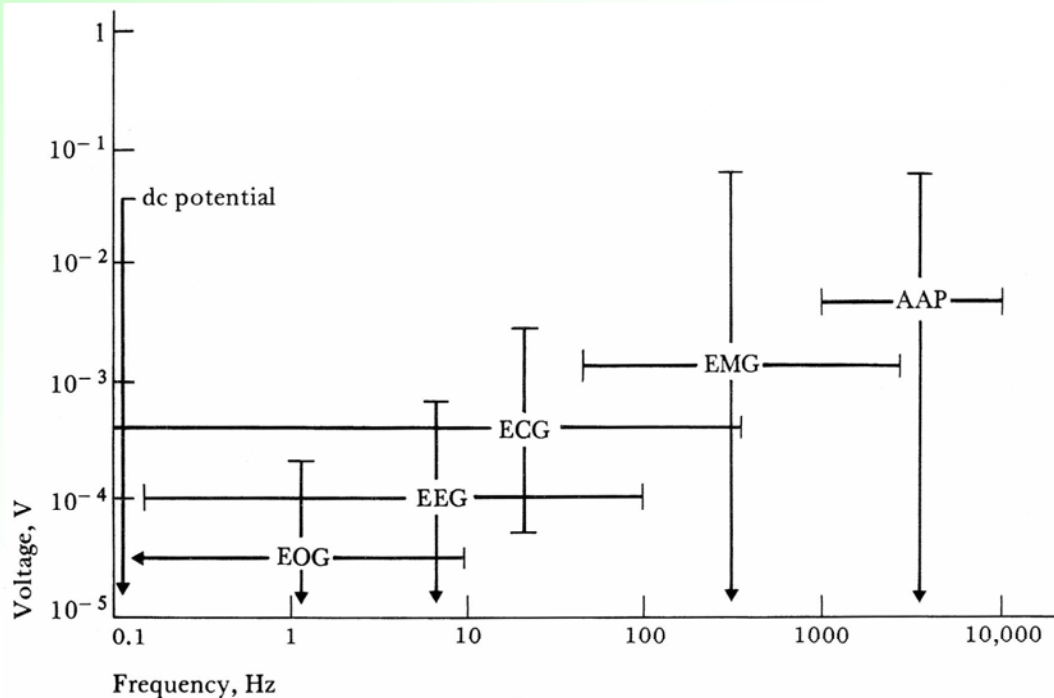


# Biopotential Amplifiers



- Basic function
  - to increase the amplitude of a weak electric signal of biological origin (next slide)
  - typically process *voltages*
    - but in some cases also process currents
- Typical bio-amp requirements
  - high input impedance -greater than 10 Mohms
  - safety: protect the organism being studied
    - careful design to prevent macro and microshocks
    - isolation and protection circuitry to limit the current through the electrode to safe level
  - output impedance of the amplifier
    - should be low to drive any external load with minimal distortion
  - gain greater than 1000
    - biopotentials are typically less than a millivolt
  - most biopotential amplifiers are differential
    - signals are recorded using a bipolar electrodes which are symmetrically located
  - high common mode rejection ratio
    - biopotentials ride on a large offset signals
  - rapid calibration of the amplifier in laboratory conditions
  - adjustable gains
    - often the change in scale is automatic
    - therefore calibration of the equipment is very important

# Voltage and Frequency Range for Biopotentials


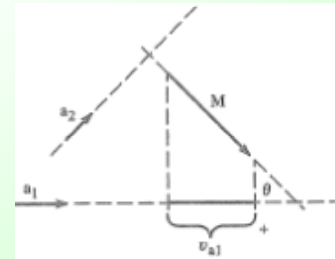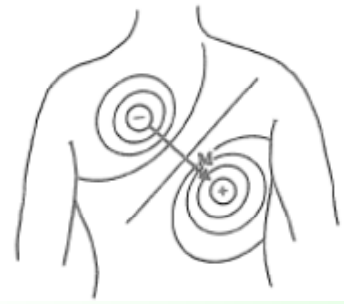
## Electrocardiograph amplifiers



- Beating heart generates electric signal
  - monitored to understand heart functions
- Measurements are functions of
  - location at which the signal is detected
  - time-dependence of the signal amplitude
- Different pairs of electrodes at different locations yield different measurements
  - hence placement is standardized
- Electrical model of heart
  - electric dipole located in a partially conducting medium (thorax)
  - dipole represented as a cardiac vector  $M$ 
    - $M$  is the dipole moment
  - during the cardiac cycle
    - magnitude and direction of the dipole vector will vary
  - electric potentials appears throughout the body and on its surface




$$v_{a1} = \mathbf{M} \cdot \mathbf{a}_1, \quad v_{a1} = |\mathbf{M}| \cos \theta$$
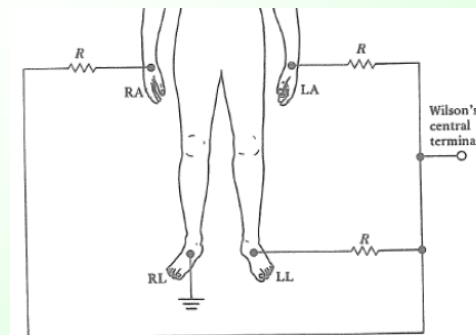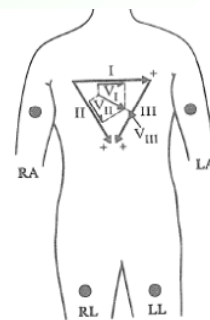
## Electrocardiograph Leads

- In clinical electrocardiography
  - more than one lead must be recorded to describe the heart's electric activity fully
  - several leads are taken in the frontal plane and the transverse plane
    - frontal plane: parallel to the back when lying
    - transverse plane: parallel to the ground when standing
- Frontal plane lead placement
  - called *Einthoven's triangle*
- Additional leads
  - unipolar measurements
    - potential measured at electrodes wrt a reference; average of the 2 electrodes
  - *Wilson central terminal*
    - three limb electrodes connected through equal-valued resistors to a common node
  - augmented leads
    - some nodes disconnected
    - increase the amplitude of measurement using



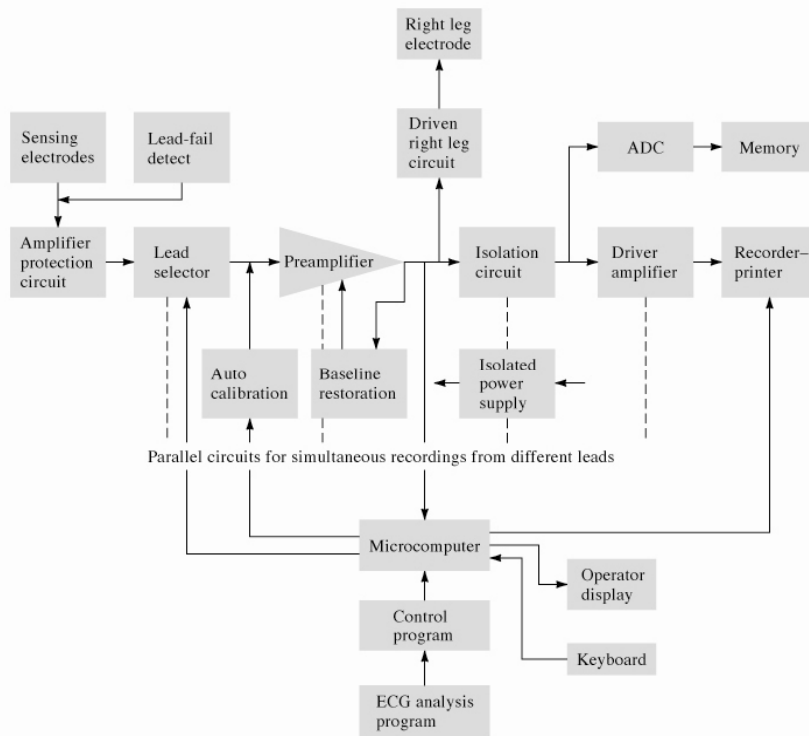
# Functional blocks of electrocardiograph



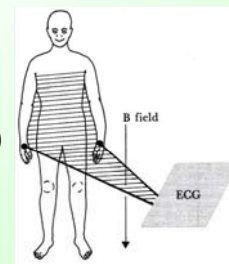
# Problems in ECG Measurement

- Frequency distortion
  - if filter specification does not match the frequency content of biopotential
  - then the result is high and low frequency distortion
- Saturation or cutoff distortion
  - high electrode offset voltage or improperly calibrated amplifiers can drive the amplifier into saturation
  - then the peaks of QRS waveforms are cut off
- Ground loops
  - if two monitoring instruments are placed at disjoint ground points
  - then small current could flow through the patient's body
- Electric/magnetic field coupling
  - open lead wires (floating connections) pick up EMI
  - long leads produce loop that picks up EMI (induces loop current)
- Interference from power lines (common mode interference)
  - can couple onto ECG signal



60Hz supply noise

Coupled to ECG

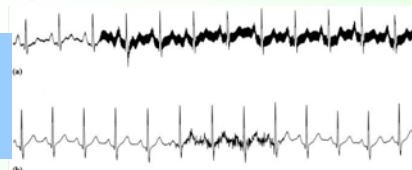

# Interference Reduction Techniques

Common-mode voltages can be responsible for much of the interference in biopotential amplifiers.

- Solution 1:
  - amplifier with a very high common-mode rejection
- Solution 2:
  - eliminate the source of interference

## Ways to eliminate interference

- Use shielding techniques
  - electrostatic shielding: Place a grounded conducting plane between the source of the electric field and the measurement system
    - very important for EEG measurement
- Magnetic shield
  - use high permeability materials (sheet steel)
- Use twisted cables to reduce magnetic flux, reduce lead loop area

# Differential Amplifier

## • One-amp differential amplifier

- gain determination
  - Rule 1: virtual short at op-amp inputs
  - Rule 2: no current into op-amp

$$v_5 = \frac{v_{in+} R_4}{R_3 + R_4} \quad i = \frac{v_{in-} - v_5}{R_3} = \frac{v_5 - v_o}{R_4}$$



$$\rightarrow v_o = \frac{(v_{in+} - v_{in-}) R_4}{R_3}$$

Gain of differential amplifier (not gain of op-amp)  $\frac{v_o}{v_{in}} = \frac{R_4}{R_3} = G_d$
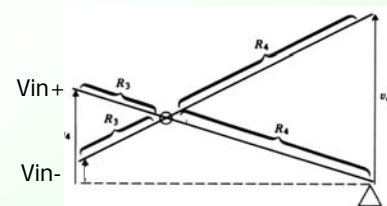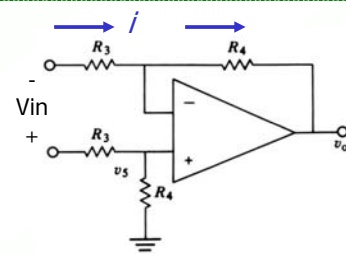
## • characteristics

- no common mode gain,  $G_c = 1$
- input resistance of the diff. amp is lower than ideal op-amp
  - OK for low resistance sources (like Wheatstone bridge), but not good for many biomedical applications

**common mode rejection ratio:**  $CMRR = \frac{G_d}{G_c}$




# Differential Amplifier

- How do we fix low input resistance of 1-op-amp diff amp?


- Option 1: Add voltage follower to each input

- Problem: ?

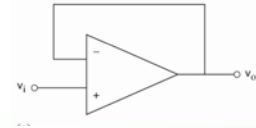


- Option 2: Add non-inverting amp at each input

- Provides additional gain
- Problem: ?

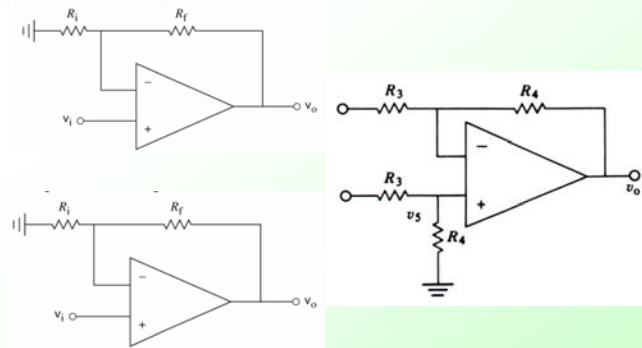
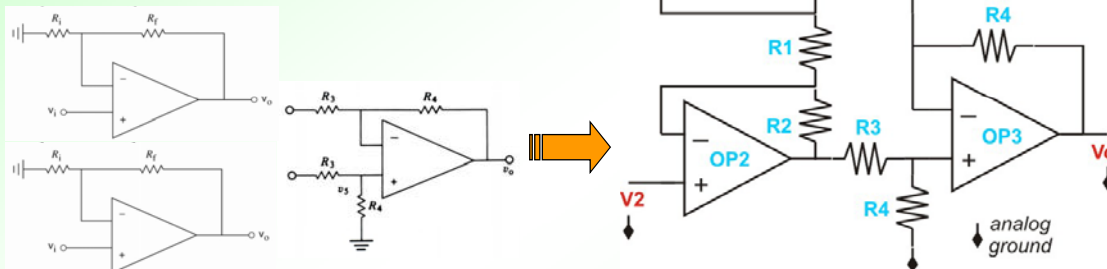
# Instrumentation Amplifier

- Better option:
  - connect  $R_i$ 's of input amps together
  - eliminate ground connection



- This 3-op-amp circuit is called an *instrumentation amplifier*


- Input stage characteristics

- low common-mode gain -rejects common mode voltages (noise)
- high input impedance

- input stage gain adjusted by  $R_1$   $G_d = \frac{v_3 - v_4}{v_1 - v_2} = \frac{2R_2 + R_1}{R_1}$
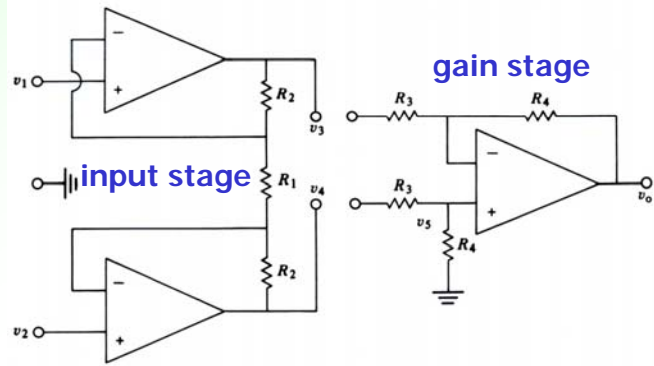
# Instrumentation Amplifier


- Input stage
  - high input impedance
    - buffers gain stage
  - no common mode gain
  - can have differential gain
- Gain stage
  - differential gain, low input impedance
- Overall amplifier
  - amplifies only the differential component
    - high common mode rejection ratio
  - high input impedance suitable for biopotential electrodes with high output impedance



*total differential gain*

$$G_d = \frac{2R_2 + R_1}{R_1} \left( \frac{R_4}{R_3} \right)$$

# ECG Amplifier

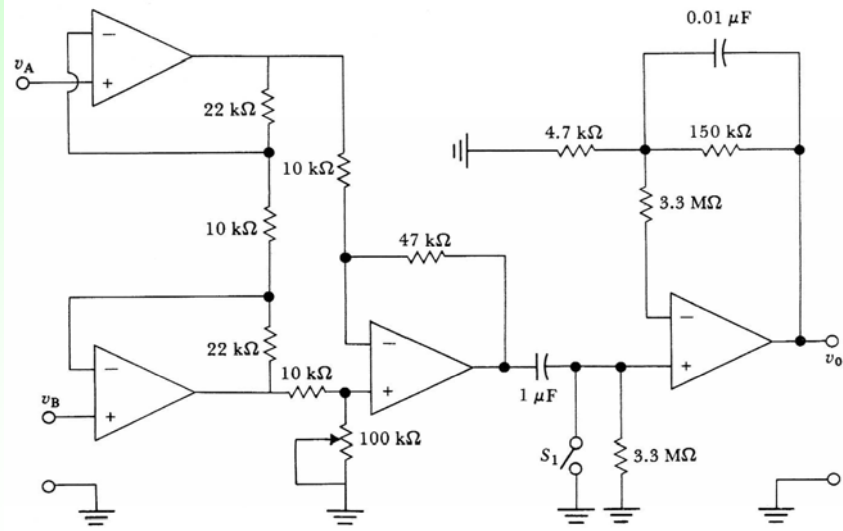


*instrumentation amplifier*      *HPF*      *non-inverting amp*

With 776 op amps, the circuit was found to have a CMRR of 86 dB at 100 Hz and a noise level of 40 mV peak to peak at the output. The frequency response was 0.04 to 150 Hz for ±3 dB and was flat over 4 to 40 Hz. The total gain is 25 (instrument amp) x 32 (non-inverting amp) = 800.
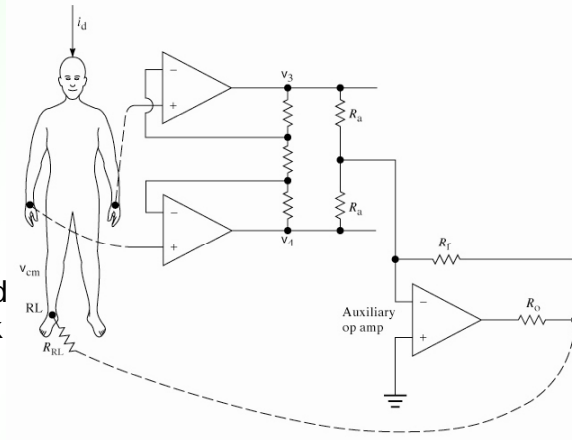
# Driven Right Leg System

- Motivation
  - reduce interference in amplifier
  - improve patient safety
- Approach
  - patient right leg tied to output of an auxiliary amp rather than ground
  - common mode voltage on body sensed by averaging resistors,  $R_a$ 's & fed back to right leg
  - provides negative feedback to reduce common mode voltage
  - if high voltage appears between patient and ground, auxiliary amp effectively un-grounds the patient to stop current flow



# Driven Right Leg System: Example

- **Problem:** Determine the common-mode voltage  $v_{cm}$  on the patient in the driven-right-leg circuit of Slide 13 when a displacement current  $i_d$  flows to the patient from the power lines. Choose appropriate values for the resistances in the circuit so that the common-mode voltage is minimal and there is only a high-resistance path to ground when the auxiliary operational amplifier saturates.
- What is  $v_{cm}$  for this circuit when  $i_d = 0.2 \mu A$ ?
- **Answer:** The equivalent circuit is shown here. Note that because the common-mode gain of the input stage is 1, and because the input stage as shown has a very high input impedance,  $v_{cm}$  at the input is isolated from the output circuit.  $R_{RL}$  represents the resistance of the right-leg electrode. Summing the currents at the negative input of the operational amplifier, we get


$$\frac{2v_{cm}}{R_a} + \frac{v_o}{R_f} = 0$$

• this gives

$$v_o = -\frac{2R_f}{R_a} v_{cm} \quad \text{but} \quad v_{cm} = R_{RL} i_d + v_o$$

• thus, substituting (1) into (2) yields
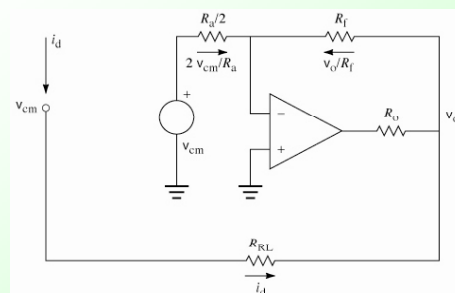
$$v_{cm} = \frac{R_{RL} i_d}{1 + 2R_f/R_a}$$




## Example continued

- The effective resistance between the right leg and ground is the resistance of the right-leg electrode divided by 1 plus the gain of the auxiliary operational-amplifier circuit. When the amplifier saturates, as would occur during a large transient  $v_{cm}$ , its output appears as the saturation voltage  $v_s$ . The right leg is now connected to ground through this source and the parallel resistances  $R_f$  and  $R_o$ . To limit the current,  $R_f$  and  $R_o$  should be large. Values as high as  $5\text{ M}\Omega$  are used.
- When the amplifier is not saturated, we would like  $v_{cm}$  to be as small as possible or, in other words, to be an effective low-resistance path to ground. This can be achieved by making  $R_f$  large and  $R_a$  relatively small.  $R_f$  can be equal to  $R_o$ , but  $R_a$  can be much smaller.
- A typical value of  $R_a$  would be  $25\text{ k}\Omega$ . A worst-case electrode resistance  $R_{RL}$  would be  $100\text{ k}\Omega$ . The effective resistance between the right leg and ground would then be



$$\frac{100\text{ k}\Omega}{1 + \frac{2 \times 5\text{ M}\Omega}{25\text{ k}\Omega}} = 249\ \Omega$$

- For the  $0.2\ \mu\text{A}$  displacement current, the common-mode voltage is
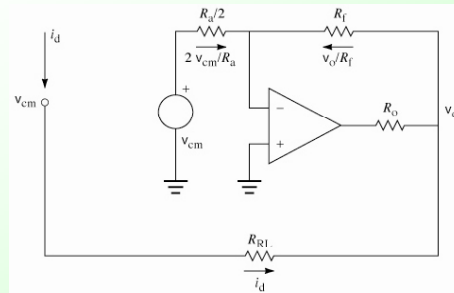
$$v_{cm} = 249\ \Omega \times 0.2\ \mu\text{A} = 50\ \mu\text{V}$$



## Compensation of electrode artifacts

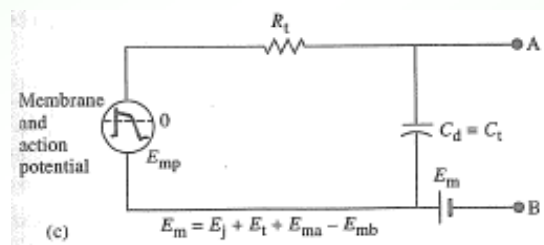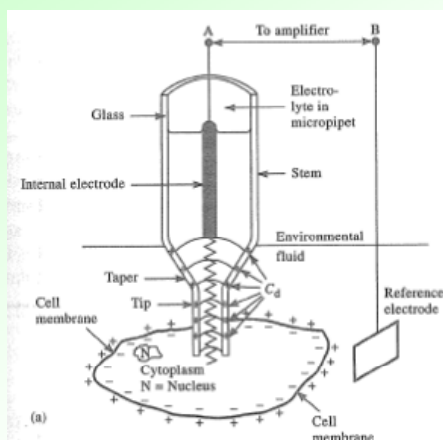

- Microelectrodes detect potentials on the order of  $50\text{-}100\text{ mV}$ .
- Small size implies high source impedance which also results in a large shunting capacitance.
- Degraded frequency response.




## Compensation of electrode artifacts

- Compensate large shunt capacitance using a positive feedback
- Circuit below realizes a negative capacitance

$$v_i = \frac{1}{C_f} \int i_1 dt + A_v v_i$$
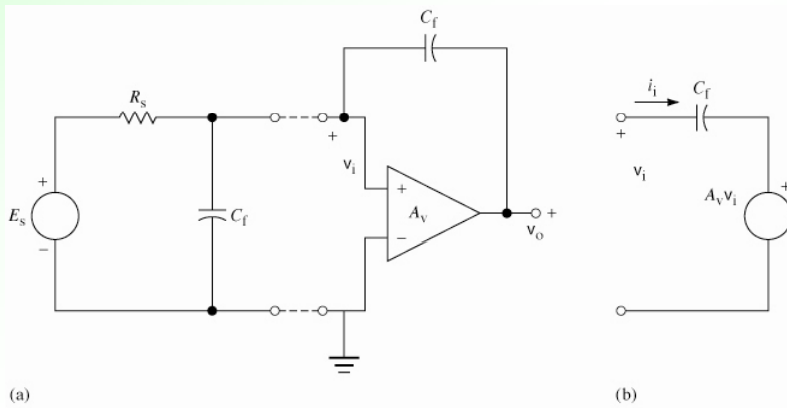
$$v_i = \frac{1}{(1 - A_v)C_f} \int i_1 dt$$



- Total capacitance

$$C = C_s + (1 - A_v)C_f$$

- Compensation criteria

$$C_s = (A_v - 1)C_f$$