

Παράρτημα Β:
Συνδυασμοί Φορτίων

Ισοδύναμη Αντίσταση (Ω)	Κλειστοί (ON) διακόπτες 1 ^{ου} Τμήματος (σε παραλληλία)			Κλειστοί (ON) διακόπτες 2 ^{ου} Τμήματος (σε παραλληλία με το 1 ^ο)			Κλειστοί (ON) διακόπτες 3 ^{ου} Τμήματος (σε παραλληλία με το 2 ^ο)		
	4400	2200	1100	4400	2200	1100	4400	2200	1100
4400	ON	off	off	-	-	-	-	-	-
2200	off	ON	off	-	-	-	-	-	-
1100	off	off	ON	-	-	-	-	-	-
1467	ON	ON	off	-	-	-	-	-	-
880	ON	off	ON	-	-	-	-	-	-
733	off	ON	ON	-	-	-	-	-	-
629	ON	ON	ON	-	-	-	-	-	-
550	ON	off	off	ON	ON	ON	-	-	-
489	off	ON	off	ON	ON	ON	-	-	-
440	off	off	ON	off	ON	ON	-	-	-
400	off	off	ON	ON	ON	ON	-	-	-
367	ON	off	ON	ON	ON	ON	-	-	-
338	off	ON	ON	ON	ON	ON	-	-	-
314	ON	ON	ON	ON	ON	ON	-	-	-
293	ON	off	off	ON	ON	ON	ON	ON	ON
275	off	ON	off	ON	ON	ON	ON	ON	ON
259	off	off	ON	off	ON	ON	ON	ON	ON
244	off	off	ON	ON	ON	ON	ON	ON	ON
232	ON	off	ON	ON	ON	ON	ON	ON	ON
220	off	ON	ON	ON	ON	ON	ON	ON	ON
210	ON	ON	ON	ON	ON	ON	ON	ON	ON

Σημείωση: Αρκετοί άλλοι συνδυασμοί (από αυτούς που φαίνονται στον πίνακα) μπορούν να δώσουν το ίδιο αποτέλεσμα.

