

ELGC06

3-phase Inverters

ORGANIZATION

I. Voltage Source Inverter (VSI)

A. Six-Step VSI

B. Pulse-Width Modulated VSI

II. PWM Methods

A. Sine PWM

B. Hysteresis (Bang-bang)

C. Space Vector PWM

III. References

I. Voltage Source Inverter (VSI)

A. Six-Step VSI (1)

➤ Six-Step three-phase Voltage Source Inverter

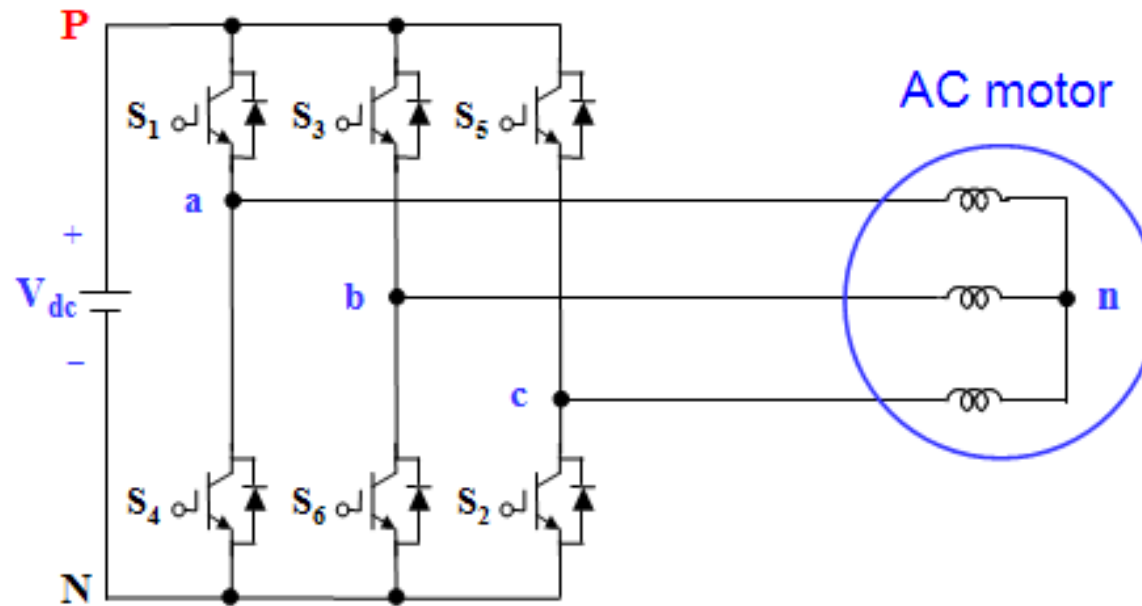


Fig. 1 Three-phase voltage source inverter.

I. Voltage Source Inverter (VSI)

A. Six-Step VSI (2)

➤ Gating signals, switching sequence and line to negative voltages

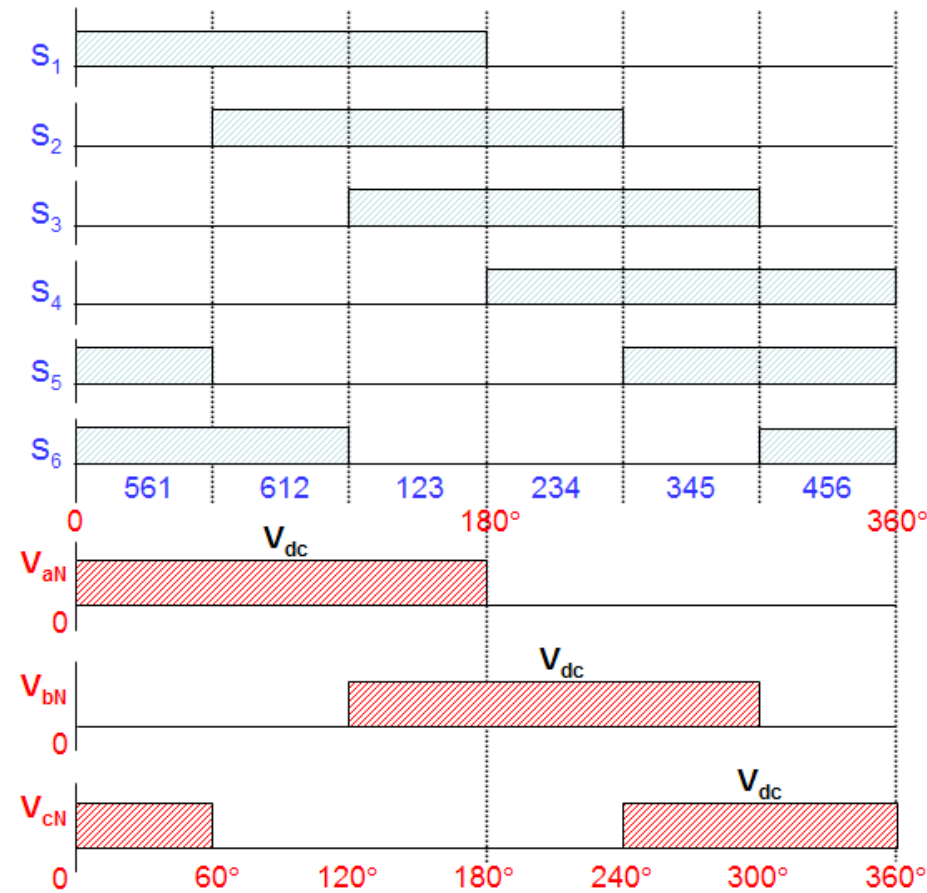


Fig. 2 Waveforms of gating signals, switching sequence, line to negative voltages for six-step voltage source inverter.

I. Voltage Source Inverter (VSI)

A. Six-Step VSI (3)

➤ **Switching Sequence:**

561 (V_1) → 612 (V_2) → 123 (V_3) → 234 (V_4) → 345 (V_5) → 456 (V_6) → 561 (V_1)

where, 561 means that S_5 , S_6 and S_1 are switched on

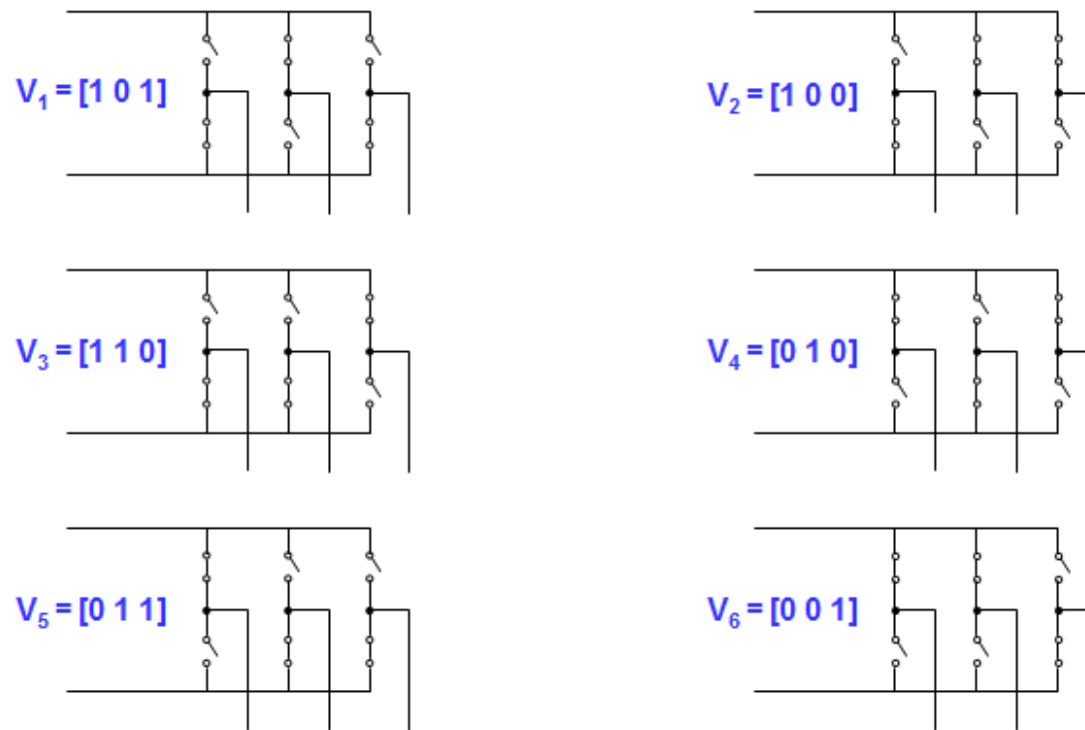


Fig. 3 Six inverter voltage vectors for six-step voltage source inverter.

I. Voltage Source Inverter (VSI)

A. Six-Step VSI (4)

➤ Line to line voltages (V_{ab} , V_{bc} , V_{ca}) and line to neutral voltages (V_{an} , V_{bn} , V_{cn})

◆ Line to line voltages

$$\Rightarrow V_{ab} = V_{aN} - V_{bN}$$

$$\Rightarrow V_{bc} = V_{bN} - V_{cN}$$

$$\Rightarrow V_{ca} = V_{cN} - V_{aN}$$

◆ Phase voltages

$$\Rightarrow V_{an} = \frac{2}{3}V_{aN} - \frac{1}{3}V_{bN} - \frac{1}{3}V_{cN}$$

$$\Rightarrow V_{bn} = -\frac{1}{3}V_{aN} + \frac{2}{3}V_{bN} - \frac{1}{3}V_{cN}$$

$$\Rightarrow V_{cn} = -\frac{1}{3}V_{aN} - \frac{1}{3}V_{bN} + \frac{2}{3}V_{cN}$$

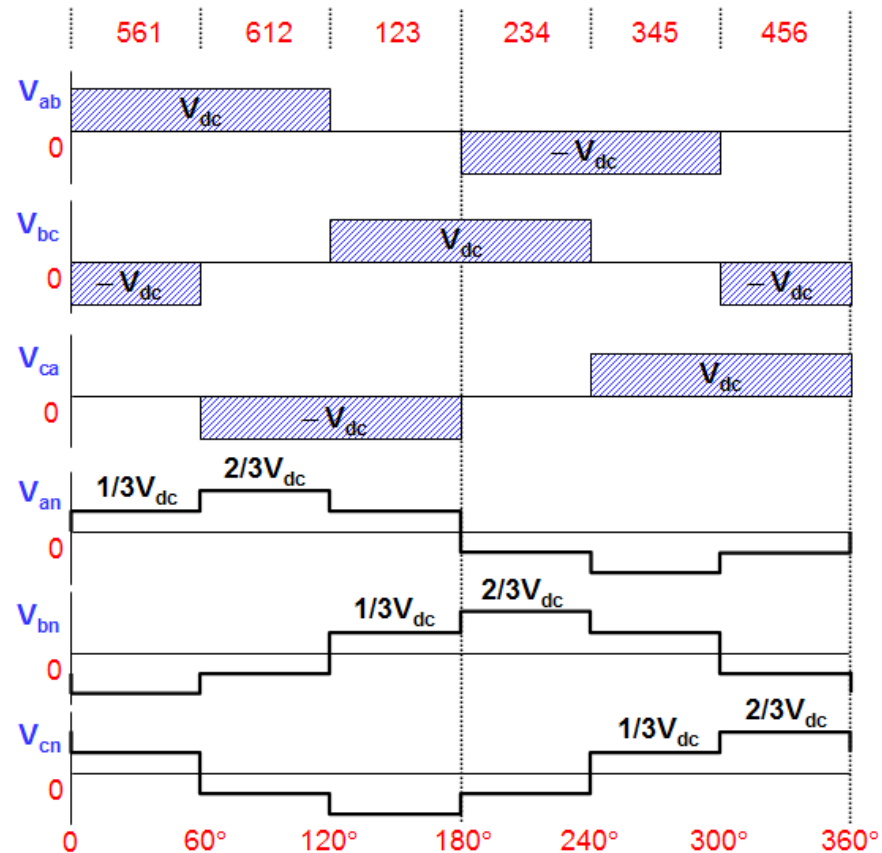


Fig. 4 Waveforms of line to neutral (phase) voltages and line to line voltages for six-step voltage source inverter.

I. Voltage Source Inverter (VSI)

A. Six-Step VSI (5)

➤ **Amplitude of line to line voltages (V_{ab} , V_{bc} , V_{ca})**

◆ **Fundamental Frequency Component (V_{ab})₁**

$$(V_{ab})_1(\text{rms}) = \frac{\sqrt{3}}{\sqrt{2}} \frac{4}{\pi} \frac{V_{dc}}{2} = \frac{\sqrt{6}}{\pi} V_{dc} \approx 0.78V_{dc}$$

◆ **Harmonic Frequency Components (V_{ab})_h**

: amplitudes of harmonics decrease inversely proportional to their harmonic order

$$(V_{ab})_h(\text{rms}) = \frac{0.78}{h} V_{dc}$$

where, $h = 6n \pm 1$ ($n = 1, 2, 3, \dots$)

I. Voltage Source Inverter (VSI)

A. Six-Step VSI (6)

➤ Characteristics of Six-step VSI

- ♦ It is called “six-step inverter” because of the presence of six “steps” in the line to neutral (phase) voltage waveform
- ♦ Harmonics of order three and multiples of three are absent from both the line to line and the line to neutral voltages and consequently absent from the currents
- ♦ Output amplitude in a three-phase inverter can be controlled by only change of DC-link voltage (V_{dc})

I. Voltage Source Inverter (VSI)

B. Pulse-Width Modulated VSI (1)

➤ Objective of PWM

- ◆ Control of inverter output voltage**
- ◆ Reduction of harmonics**

➤ Disadvantages of PWM

- ◆ Increase of switching losses due to high PWM frequency**
- ◆ Reduction of available voltage**
- ◆ EMI problems due to high-order harmonics**

I. Voltage Source Inverter (VSI)

B. Pulse-Width Modulated VSI (2)

➤ Pulse-Width Modulation (PWM)

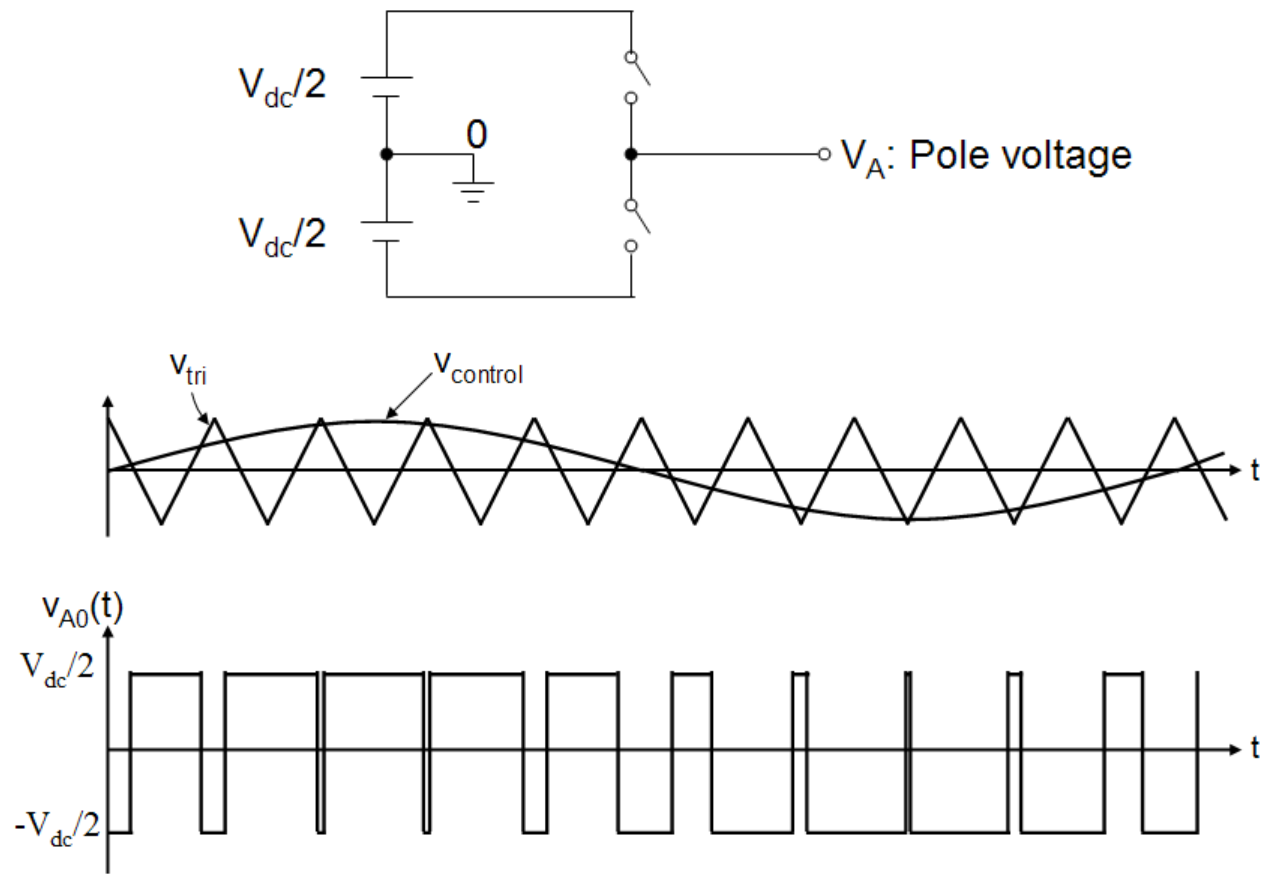


Fig. 5 Pulse-width modulation.

I. Voltage Source Inverter (VSI)

B. Pulse-Width Modulated VSI (3)

➤ Inverter output voltage

♦ When $v_{\text{control}} > v_{\text{tri}}$, $V_{A0} = V_{\text{dc}}/2$

♦ When $v_{\text{control}} < v_{\text{tri}}$, $V_{A0} = -V_{\text{dc}}/2$

➤ Control of inverter output voltage

♦ PWM frequency is the same as the frequency of v_{tri}

♦ Amplitude is controlled by the peak value of v_{control}

♦ Fundamental frequency is controlled by the frequency of v_{control}

➤ Modulation Index (m)

$$\therefore m = \frac{v_{\text{control}}}{v_{\text{tri}}} = \frac{\text{peak of } (V_{A0})_1}{V_{\text{dc}}/2},$$

where, $(V_{A0})_1$: fundamental frequency component of V_{A0}

II. PWM METHODS

A. Sine PWM (1)

➤ Three-phase inverter

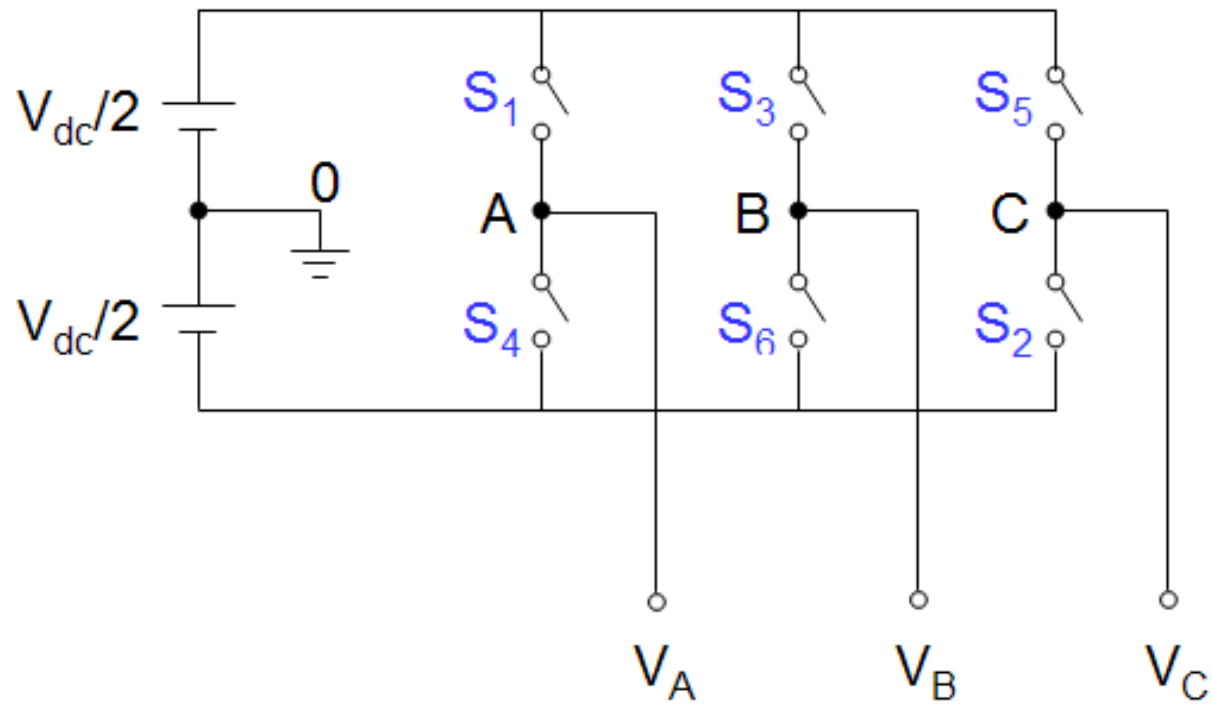


Fig. 6 Three-phase Sine PWM inverter.

II. PWM METHODS

A. Sine PWM (2)

➤ Three-phase sine PWM waveforms

◆ Frequency of v_{tri} and $v_{control}$

⇒ Frequency of $v_{tri} = f_s$

⇒ Frequency of $v_{control} = f_1$

where, $f_s =$ PWM frequency

$f_1 =$ Fundamental frequency

◆ Inverter output voltage

⇒ When $v_{control} > v_{tri}$, $V_{A0} = V_{dc}/2$

⇒ When $v_{control} < v_{tri}$, $V_{A0} = -V_{dc}/2$

where, $V_{AB} = V_{A0} - V_{B0}$

$V_{BC} = V_{B0} - V_{C0}$

$V_{CA} = V_{C0} - V_{A0}$

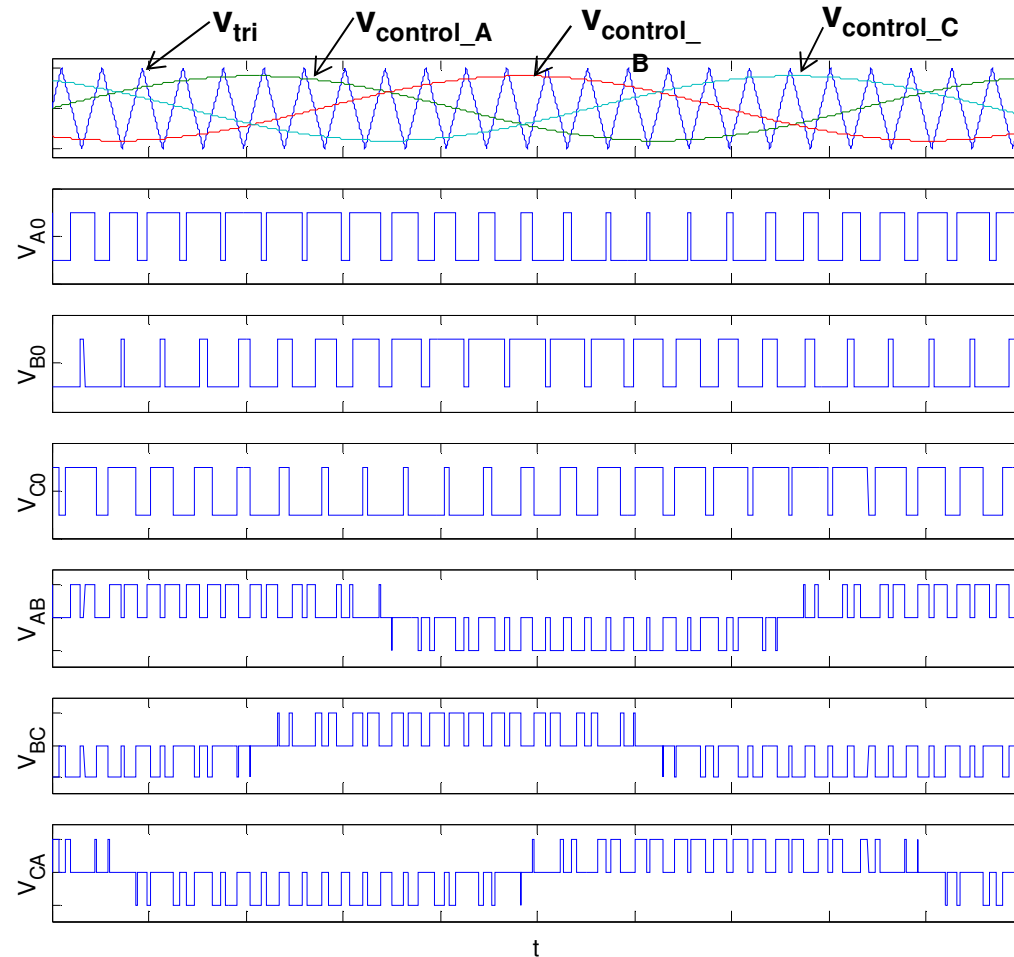


Fig. 7 Waveforms of three-phase sine PWM inverter.

II. PWM METHODS

A. Sine PWM (3)

➤ Amplitude modulation ratio (m_a)

$$\therefore m_a = \frac{\text{peak amplitude of } v_{\text{control}}}{\text{amplitude of } v_{\text{tri}}} = \frac{\text{peak value of } (V_{A0})_1}{V_{dc} / 2},$$

where, $(V_{A0})_1$: fundamental frequency component of V_{A0}

$$U_{ab1,\text{rms}} = m_a \frac{U_i}{2} \sqrt{\frac{3}{2}}, \quad U_i = 0,95 U_{i,\text{rms}} \sqrt{2}, \quad U_{i,\text{rms}} \text{ the rms line voltage value (phase or phase to phase)}$$

➤ Frequency modulation ratio (m_f)

$$m_f = \frac{f_s}{f_1}, \quad \text{where, } f_s = \text{PWM frequency and } f_1 = \text{fundamental frequency}$$

♦ m_f should be an odd integer

⇒ if m_f is not an integer, there may exist subharmonics at output voltage

⇒ if m_f is not odd, DC component may exist and even harmonics are present at output voltage

♦ m_f should be a multiple of 3 for three-phase PWM inverter

⇒ An odd multiple of 3 and even harmonics are suppressed

II. PWM METHODS

B. Hysteresis (Bang-bang) PWM (1)

- Three-phase inverter for hysteresis Current Control

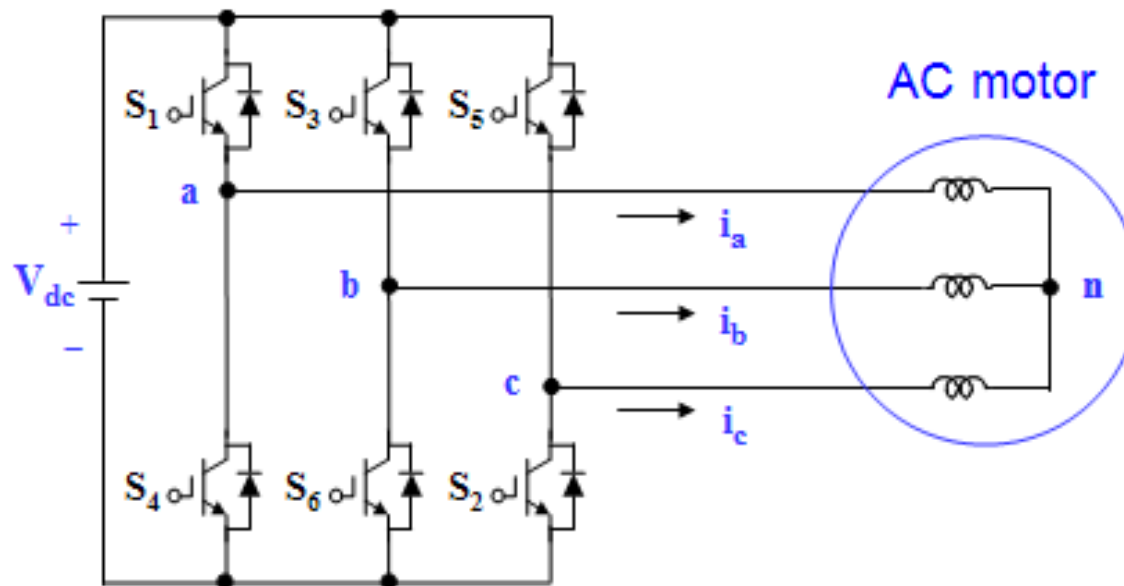


Fig. 8 Three-phase inverter for hysteresis current control.

II. PWM METHODS

B. Hysteresis (Bang-bang) PWM (2)

➤ Hysteresis Current Controller

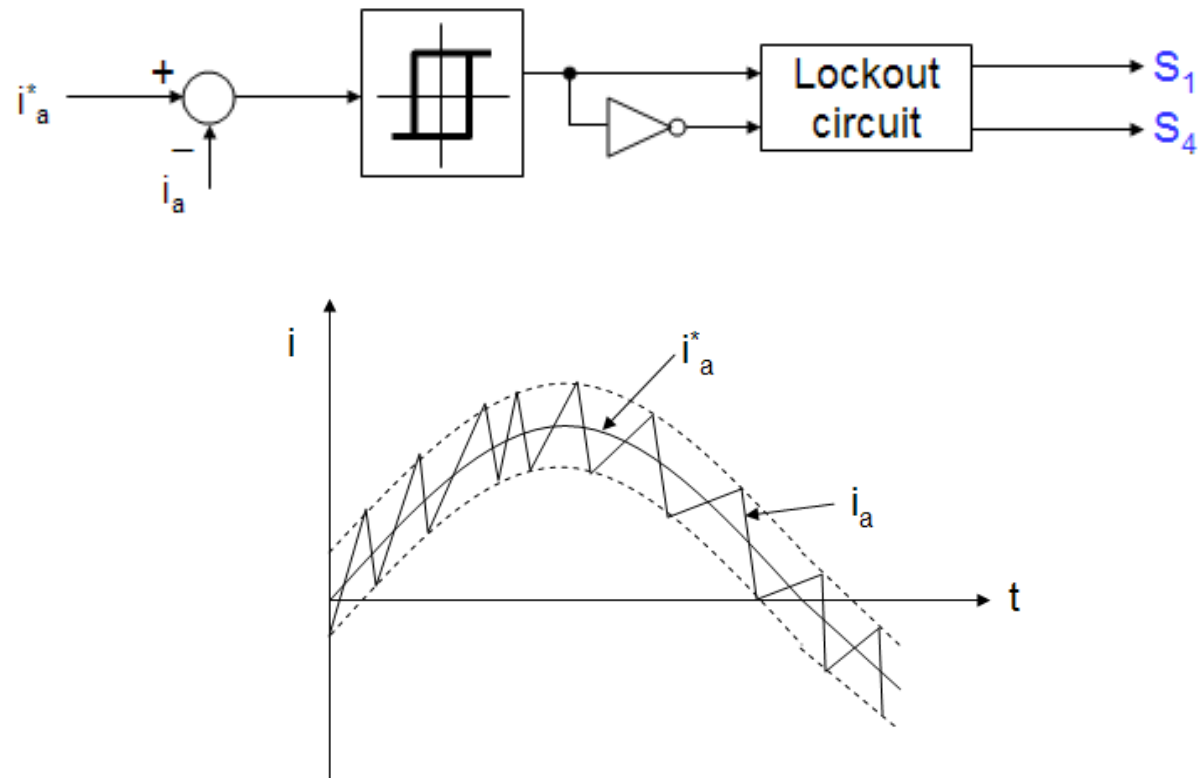


Fig. 9 Hysteresis current controller at Phase "a".

II. PWM METHODS

B. Hysteresis (Bang-bang) PWM (3)

➤ Characteristics of hysteresis Current Control

◆ Advantages

- ⇒ Excellent dynamic response
- ⇒ Low cost and easy implementation

◆ Drawbacks

- ⇒ Large current ripple in steady-state
- ⇒ Variation of switching frequency
- ⇒ No intercommunication between each hysteresis controller of three phases and hence no strategy to generate zero-voltage vectors.
As a result, the switching frequency increases at lower modulation index and the signal will leave the hysteresis band whenever the zero vector is turned on.
- ⇒ The modulation process generates subharmonic components