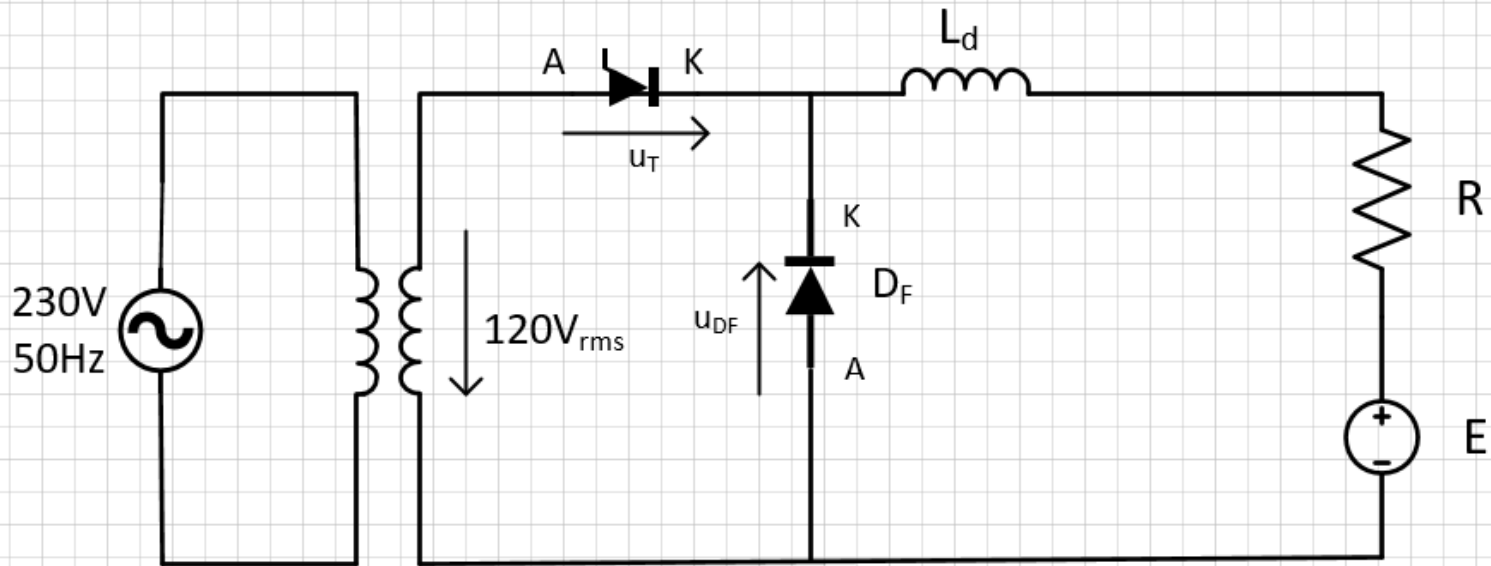


1. Σχεδιασμός Φορτιστή 1 παλμού



$E=48V$
 $I_{ch}=12A$
 $R=200m\Omega$


$$\hat{i} = 125\% \cdot I_{ch}, i_{min} = 75\% \cdot I_{ch}$$

Η D_F άγει για $\varphi \geq \pi, \varphi \leq 2\pi + \alpha$ (Συνεχής Αγωγή)


Το T άγει για $\alpha \leq \varphi \leq \pi$

ι) Υπολογισμός α, γ

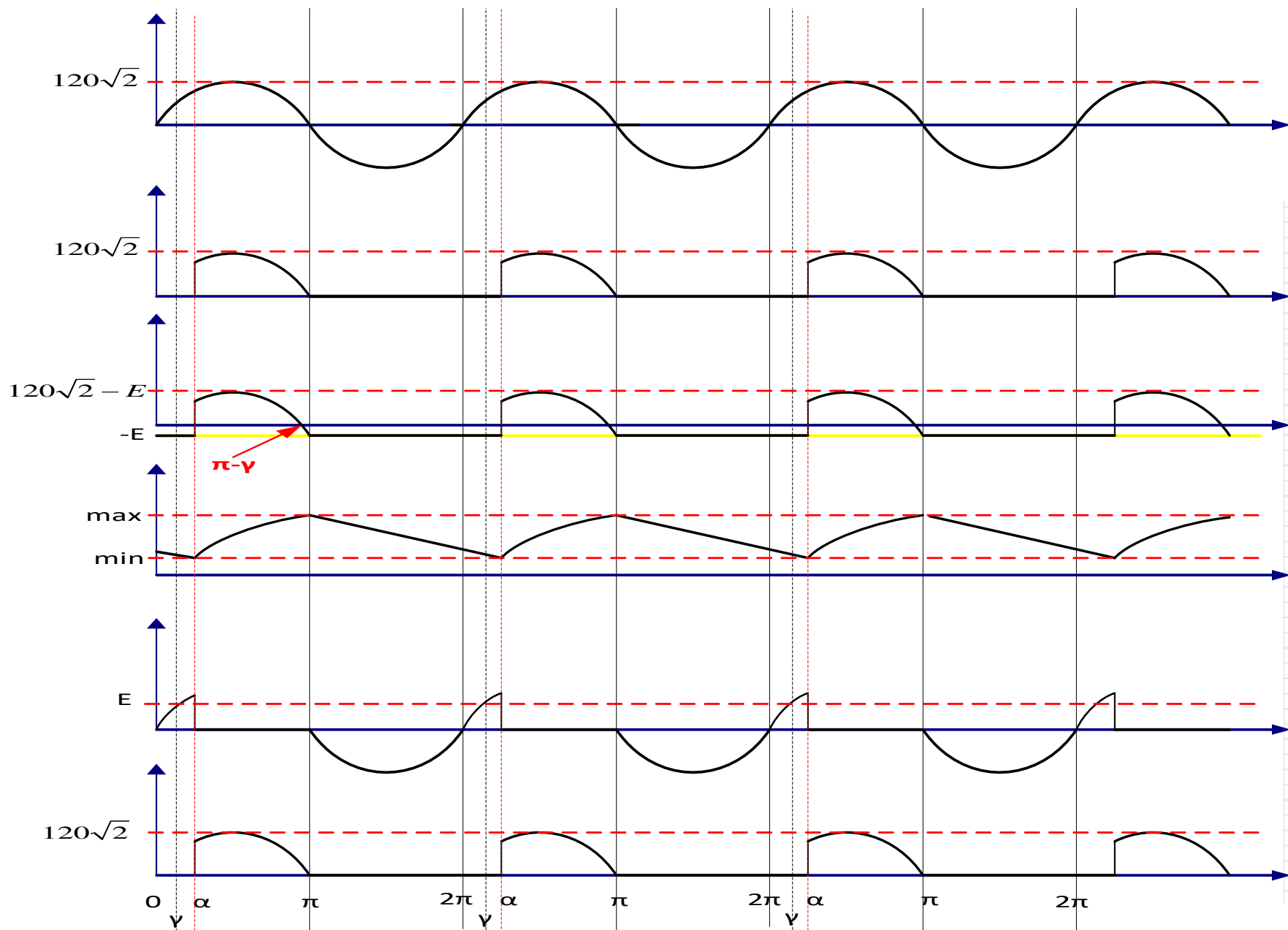- $\gamma = \sin^{-1} \frac{E}{V_{2,rms} \sqrt{2}} = \sin^{-1} \frac{48}{120\sqrt{2}} \Rightarrow \gamma = 16,4^\circ$
- $V_0 = I_{ch} \cdot R + E = 12A \cdot 200m\Omega + 48V \Rightarrow V_0 = 50,4V$
- $V_0^{(E=0)} = \frac{1}{2\pi} V_{2,rms} \sqrt{2} [1 + \cos\alpha] \Rightarrow \cos\alpha = \frac{\pi\sqrt{2}V_0}{V_{2,rms}} - 1 = 1,86 - 1 = 0,86$
 $\Rightarrow \alpha = 30,7^\circ$



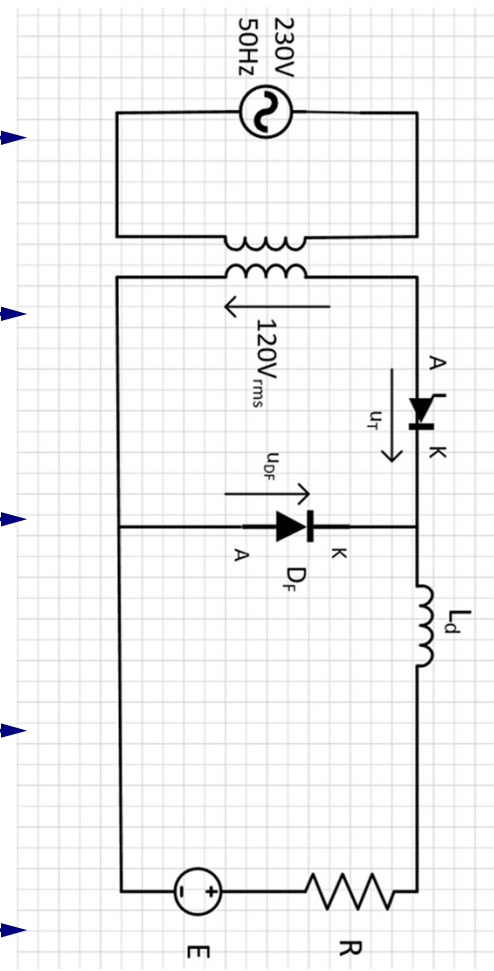ii) Σχεδιασμός $u_2(t)$,
 $u_0(t)$, $u_{Ld}(t)$, $i_{ch}(t)$,
 $u_T(t)$, $u_{DF}(t)$ ($i_{ch}R \cong 0$)



iii) Υπολογισμός του συντελεστή αυτεπαγωγής L_d

- $$a \leq \varphi \leq \pi: u_2 - E = L_d \frac{di_{ch}}{dt} \Rightarrow -I_\emptyset + i_{ch}(\varphi) =$$

$$\frac{1}{x_L} \left[\int_a^\varphi \sqrt{2} V_{2,rms} \sin \varphi d\varphi - \int_a^\varphi E d\varphi \right] \Rightarrow i_{ch}(\varphi) =$$

$$= \frac{\sqrt{2} V_{2,rms} (\cos a - \cos \varphi) - E(\varphi - a)}{x_L} + I_\emptyset$$
- $$\hat{i} = i_{ch}(\pi - \gamma) = I_\emptyset + \frac{\sqrt{2} V_{2,rms} (\cos a + \cos \gamma) - E(\pi - \gamma - a)}{x_L}$$
- $$i_{min} = i_{ch}(a) = I_\emptyset$$
- $$\Delta i = \hat{i} - i_{min} = 0,5 I_{ch} = \frac{\sqrt{2} V_{2,rms} (\cos a + \cos \gamma) - E(\pi - a - \gamma)}{x_L} \Rightarrow$$

$$x_L = \frac{120\sqrt{2}(\cos 30,7 + \cos 16,4) - 48(\pi - 0,26\pi)}{6} = \frac{120\sqrt{2}(0,86 + 0,96) - 48 \cdot 0,74 \cdot \pi}{6} = \frac{308,8 - 111,5}{6} \Rightarrow$$

$$x_L = 32,9 \Omega$$


Άρα: $L_d = \frac{x_L}{314} = \frac{32,9}{314} H \Rightarrow L_d = 105 mH$

iv) Υπολογισμός των η , pf_2 για $L_d \rightarrow \infty$, I_{avg} , I_{rms}

$$L_d \rightarrow \infty \Rightarrow i_{\text{ch}} = I_{\text{ch}}, i_{\text{T}} = \begin{cases} I_{\text{ch}}, & a \leq \varphi \leq \pi \\ 0, & \text{αλλού} \end{cases}, i_{\text{DF}} = \begin{cases} 0 & , & a \leq \varphi \leq \pi \\ I_{\text{ch}}, & \pi \leq \varphi \leq 2\pi + \alpha \end{cases}$$

- $I_{\text{T}} = I_{\text{ch}} \frac{\pi - \alpha}{2\pi} = I_{\text{ch}} \frac{0,83}{2} \Rightarrow I_{\text{T}} = 0,415 I_{\text{ch}} \Rightarrow I_{\text{T}} \simeq 5\text{A}$
- $I_{\text{DF}} = I_{\text{CH}} - I_{\text{T}} = 7\text{A}$
- $I_{\text{T,rms}}^2 = \frac{1}{2\pi} \int_{\alpha}^{\pi} I_{\text{ch}}^2 d\varphi - I_{\text{ch}}^2 \frac{\pi - \alpha}{2\pi} = I_{\text{ch}}^2 0,415 \Rightarrow I_{\text{T,rms}} = I_{\text{ch}} \sqrt{0,415} \Rightarrow I_{\text{T,rms}} = I_{\text{ch}} \cdot 0,644 = 7,7\text{A}$
- $I_{\text{DF,rms}}^2 = I_{\text{ch}}^2 - I_{\text{T,rms}}^2 = 144 - 59,29 \Rightarrow I_{\text{DF,rms}} = 9,2\text{A}$
-
- $\eta = \frac{P_{\text{ch}}}{P_{\text{R}} + P_{\text{ch}}} = \frac{576}{12^2 \cdot 0,2 + 576} = \frac{576}{28,8 + 576} \Rightarrow \eta = 95,2\%$
-
- $S = V_{2,\text{rms}} I_{\text{T,rms}} = 120\text{V} \cdot 7,7\text{A} \Rightarrow S = 924\text{VA}$
-
- $\text{pf}_2 = \frac{P_{\text{R}} + P_{\text{ch}}}{S} = \frac{28,8 + 576}{924} \Rightarrow \text{pf} = 0,65$

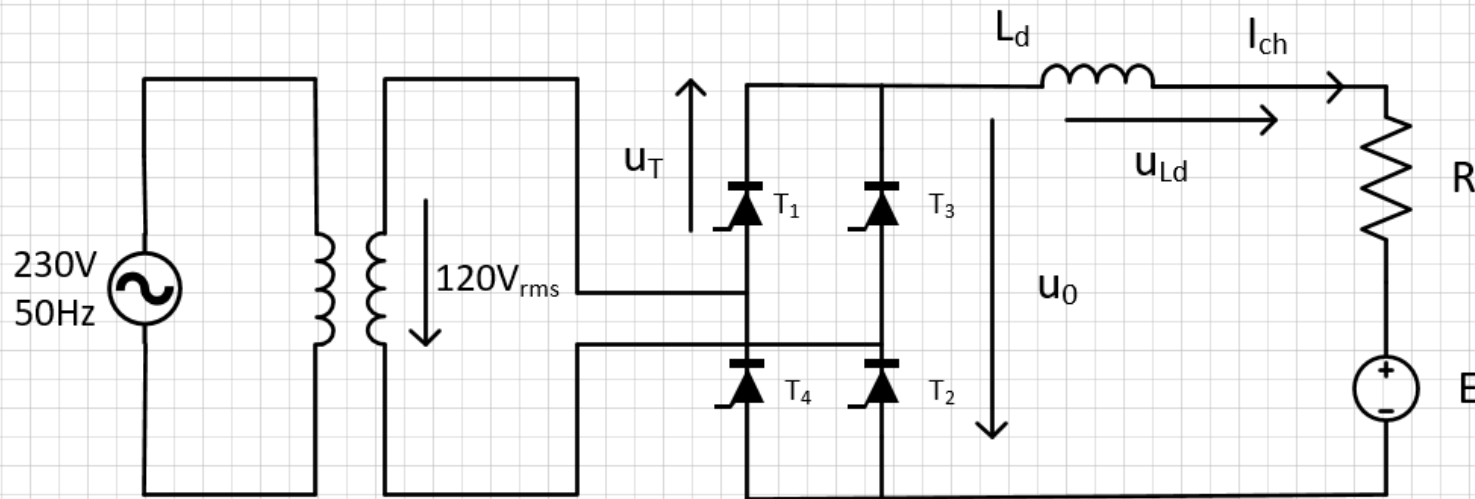2. Να επανασχεδιαστεί το κύκλωμα για πλήρη ανόρθωση



$$\hat{i} = 125\%I_{ch}$$


$$t_{min} = 0,75I_{ch}$$

$$\gamma = 16,4^\circ$$


$$V_0 = 50,4V$$

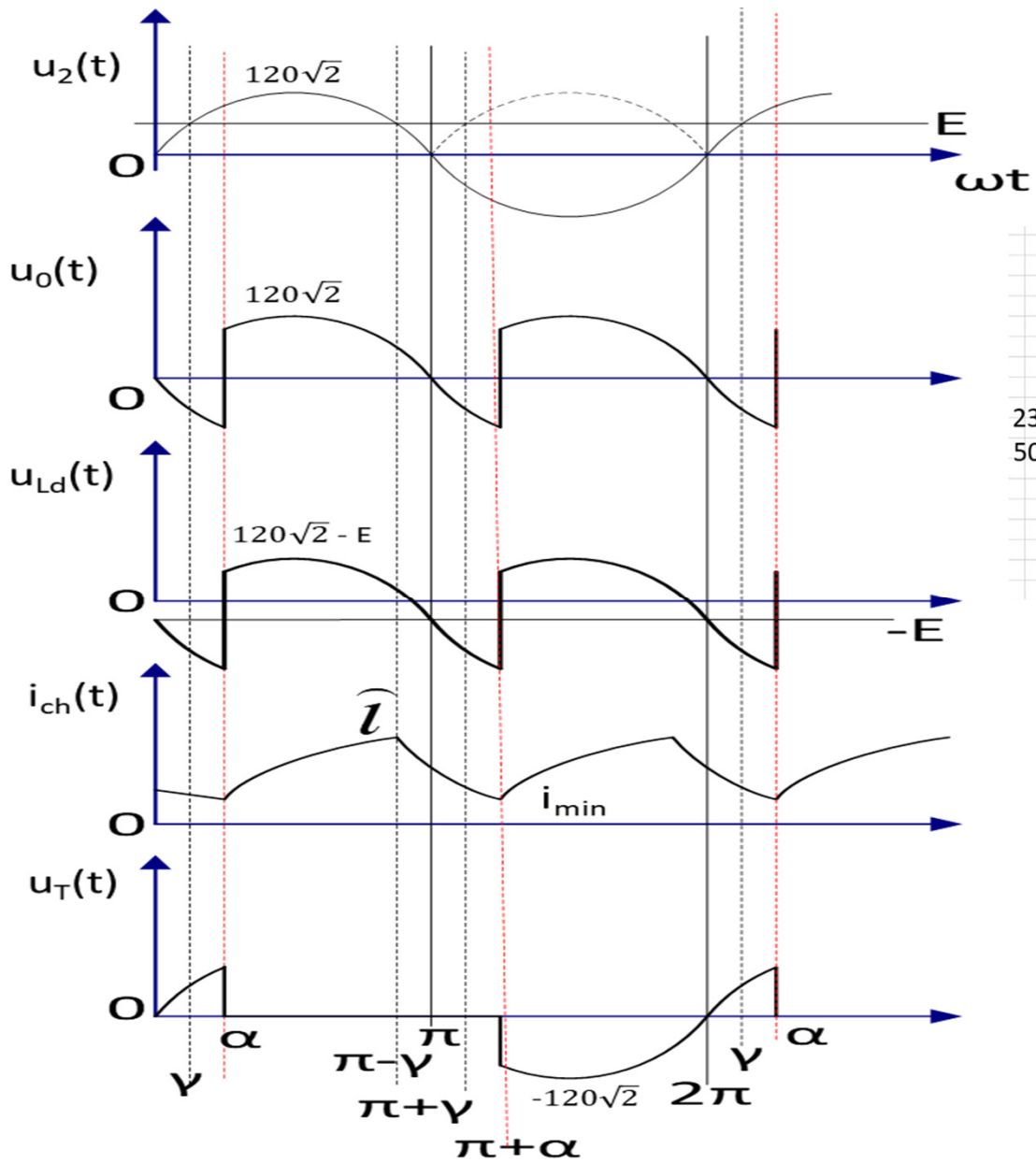i) Υπολογισμός α – Συνεχής αγωγή

$$V_0^{(E=0)} = \frac{V_{2,rms} \sqrt{2}}{\pi} \cos \alpha \Rightarrow \cos \alpha = \frac{\pi V_0}{V_{rms} \sqrt{2}} = 0,9326 \Rightarrow \alpha = 21^\circ$$



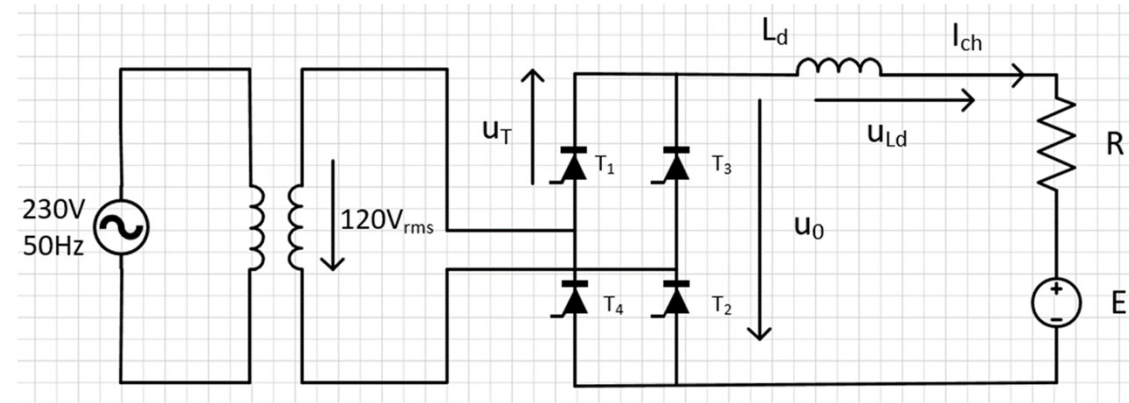ii) Σχεδιασμός $u_2(t)$, $u_0(t)$, $u_{Ld}(t)$, $i_{ch}(t)$, $u_T(t)$, ($i_{ch}R \cong 0$)



iii) Υπολογισμός της αυτεπαγωγής L_D

$$\alpha \leq \varphi \leq \pi + \alpha : i_{ch}(\varphi) = \frac{\sqrt{2}V_{2,rms} (\cos a - \cos \varphi) - E(\varphi - \alpha)}{x_L} + I_\emptyset$$

$$\Delta i = 0,5I_{ch} = i_{ch}(\pi - \gamma) - i_{ch}(a) = \frac{\sqrt{2}V_{2,rms} (\cos a + \cos \gamma) - E(\pi - \gamma - \alpha)}{x_L} \Rightarrow$$

$$x_L = \frac{120\sqrt{2}(\cos 21 + \cos 16,4) - 48(\pi - 0,21\pi)}{0,5 \cdot 12} = \frac{120\sqrt{2}(0,934 + 0,959) - 48(0,79\pi)}{6} \Rightarrow x_L = \frac{321,2 - 119,6}{6}$$

$$\Rightarrow x_L = 33,7\Omega$$

$$\text{Άρα : } L_D = \frac{x_L}{2\pi F} H = \frac{33,7}{314} H \Rightarrow L_D = 107mH$$

iv) Να υπολογιστούν τα I_{avg} , I_{rms} , η , pf_2 , για $L_D \rightarrow \infty$

- $I_T = I_{ch} \frac{\pi}{2\pi} = 0,57I_{ch} = 6A$
- $I_{T,rms} = \frac{I_{ch}}{\sqrt{2}} = 8,5A$
- $I_{2,rms} = I_{ch} = 12A$
- $\eta = \frac{P_{ch}}{P_R + P_{ch}} = \frac{576}{0,2 \cdot 12^2 + 576} = \frac{576}{604,8} = 95,2\%$
- $S_2 = V_{2,rms} I_{2,rms} = 120 \cdot 12VA = 1440VA$
- $pf_2 = \frac{604,8}{1440} = 0,42$

4. Να σχεδιαστεί το κύκλωμα με SemiConverter

i) $V_0=50,4V$, $\gamma=16,4^\circ$


- $V_0^{(E=0)} = \frac{\sqrt{2}V_{2,rms}}{\pi} (1 + \cos \alpha) \Rightarrow \cos \alpha = \frac{\pi V_0}{\sqrt{2}V_{2,rms}} - 1 = 0,933 - 1 = -0,067 \Rightarrow \alpha \simeq 90^\circ$


Διάρκεια αγωγής κάθε ζεύγους thyristor: $(\pi - \alpha)$

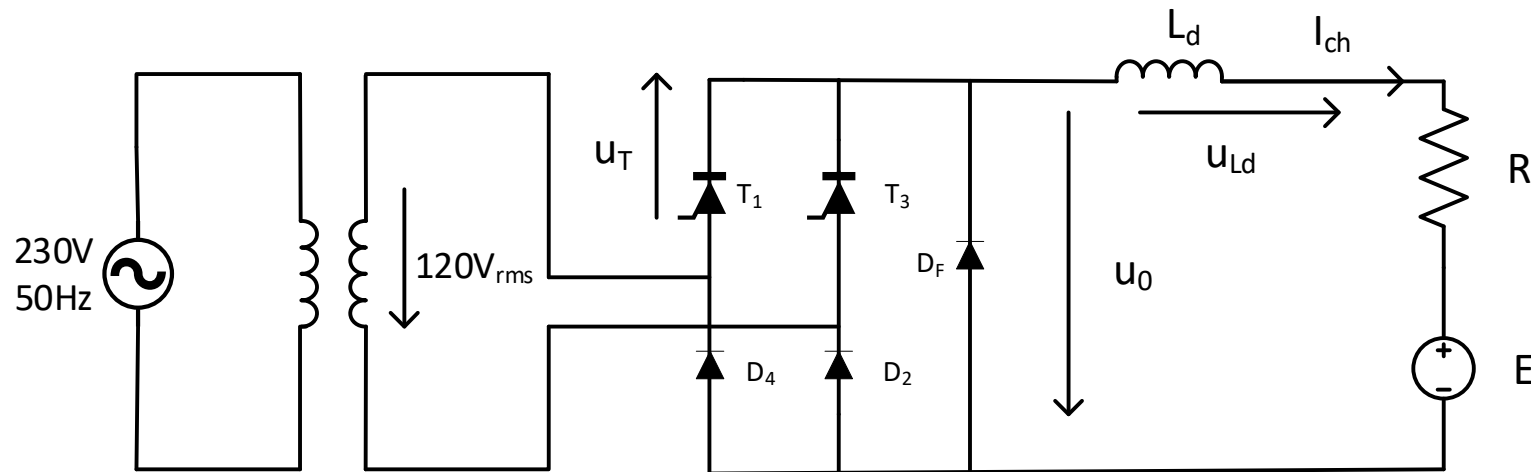ii) $\alpha \leq \varphi \leq \pi$: $i_{ch}(\varphi) = \frac{\sqrt{2}V_{2,rms}(\cos \alpha - \cos \varphi) - E(\varphi - \alpha)}{x_L} + I_\varphi$


$\Delta i = 0,5I_{ch} = i_{ch}(\pi - \gamma) - i_{ch}(\alpha) = \frac{\sqrt{2}V_{2,rms}(\cos \alpha + \cos \gamma) - E(\pi - \gamma - \alpha)}{x_L} \Rightarrow x_L = \frac{120\sqrt{2} \cdot 0,959 - 48 \cdot 0,41\pi}{0,5 \cdot 12} = \frac{162,7 - 61,8}{6} \Rightarrow x_L = 16,8\Omega$

Άρα $L_d = \frac{16,8}{314} H \Rightarrow L_d = 53,5mH$



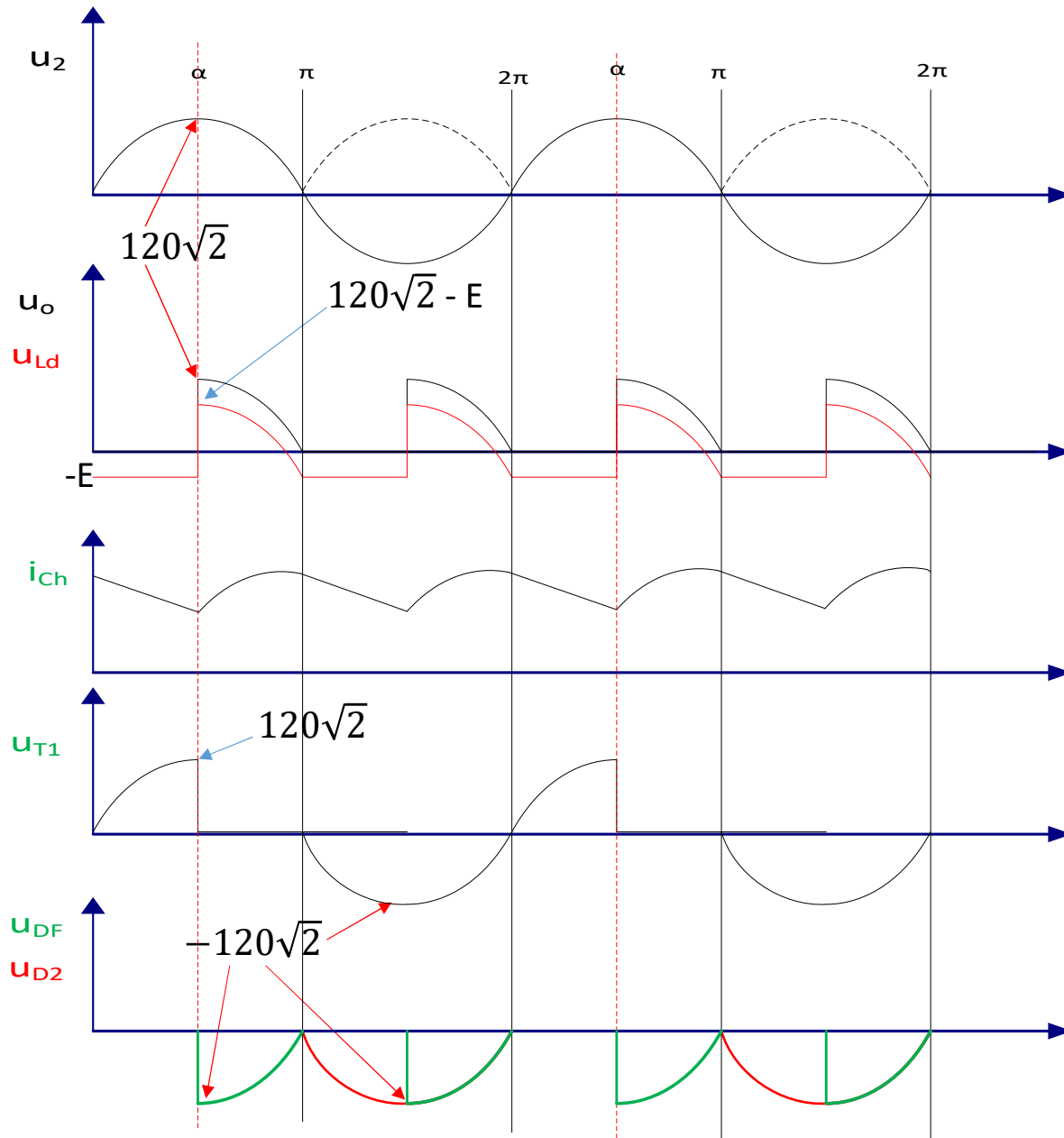

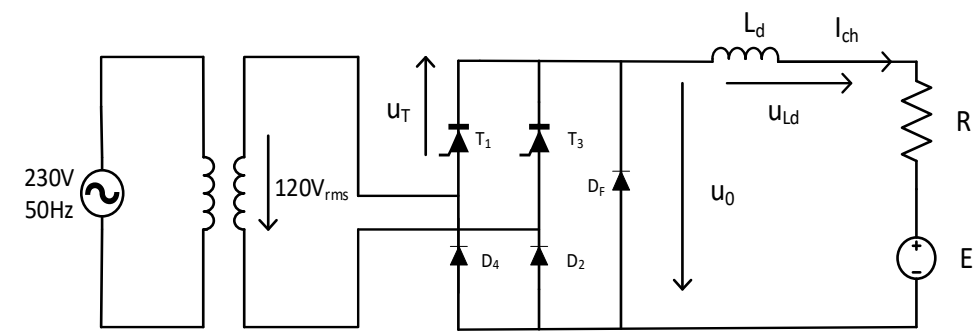iii) Να σχεδιαστούν $u_2(t)$, $u_o(t)$, $u_{Ld}(t)$, $i_{ch}(t)$, $u_T(t)$, $u_{DF}(t)$, $u_D(t)$



iv) Να υπολογιστούν τα I_{avg} , I_{rms} , η , pf_2 για $L_d \rightarrow \infty$

$$\eta=95,2\%, P_R=28,8W, P_{ch}=576W$$

- $I_T = \frac{1}{2\pi} I_{ch} (\pi - \alpha) = \frac{I_{ch}}{4} = 3A$
- $I_{DF} = 2I_T = 6A$
- $I_{T,rms}^2 = \frac{1}{2\pi} I_{ch}^2 (\pi - \alpha) \Rightarrow I_{T,rms} = \frac{I_{ch}}{2} = 6A$
- $I_{ch}^2 = 2I_{T,rms}^2 + I_{DF,rms}^2 \Rightarrow 144 = 2 \cdot 36 + I_{DF,rms}^2 \Rightarrow I_{DF,rms} = 8,5A$
- $I_{2,rms}^2 = 2I_{T,rms}^2 \Rightarrow I_{2,rms} = I_{T,rms} \sqrt{2} = \sqrt{2} \cdot 6A \Rightarrow I_{2,rms} = 8,5A$
- $S_2 = V_{2,rms} I_{2,rms} = 120V \cdot 8,5A \Rightarrow S_2 = 1020VA$
- $pf_2 = \frac{604,8}{1020} \Rightarrow pf_2 = 0,59$